

लक्ष्य वैदेय

ELECTRICAL ENGINEERING

KEY FEATURES:-

- + Live & recorded classes:
- + Class notes in PDF Form
- + Doubt Sessions
- + Practice sessions
- + Test series

Download EAD Online Classes on Playstore 

ENROLL NOW

AE | ASSISTANT ENGINEER

exam targeted:-

UPPCL AE, UPPSC, AE, UKPSC AE,
MAHATRANSCO AE AND
OTHER STATE AE / PSU EXAMS



--EAD EXPERTS



for more information contact us:-

8126989696, 7505771800, 8449597123, 8057871234



EAD ONLINE CLASSES


DC transients

Transients present in any circuit due to change in source magnitude or load elements, and it contains energy storing elements.


Energy storing Element \rightarrow Inductor \rightarrow mag. form
 Capacitor \rightarrow Electrostatic form.

In Pure resistive circuit \rightarrow Transients are not present.

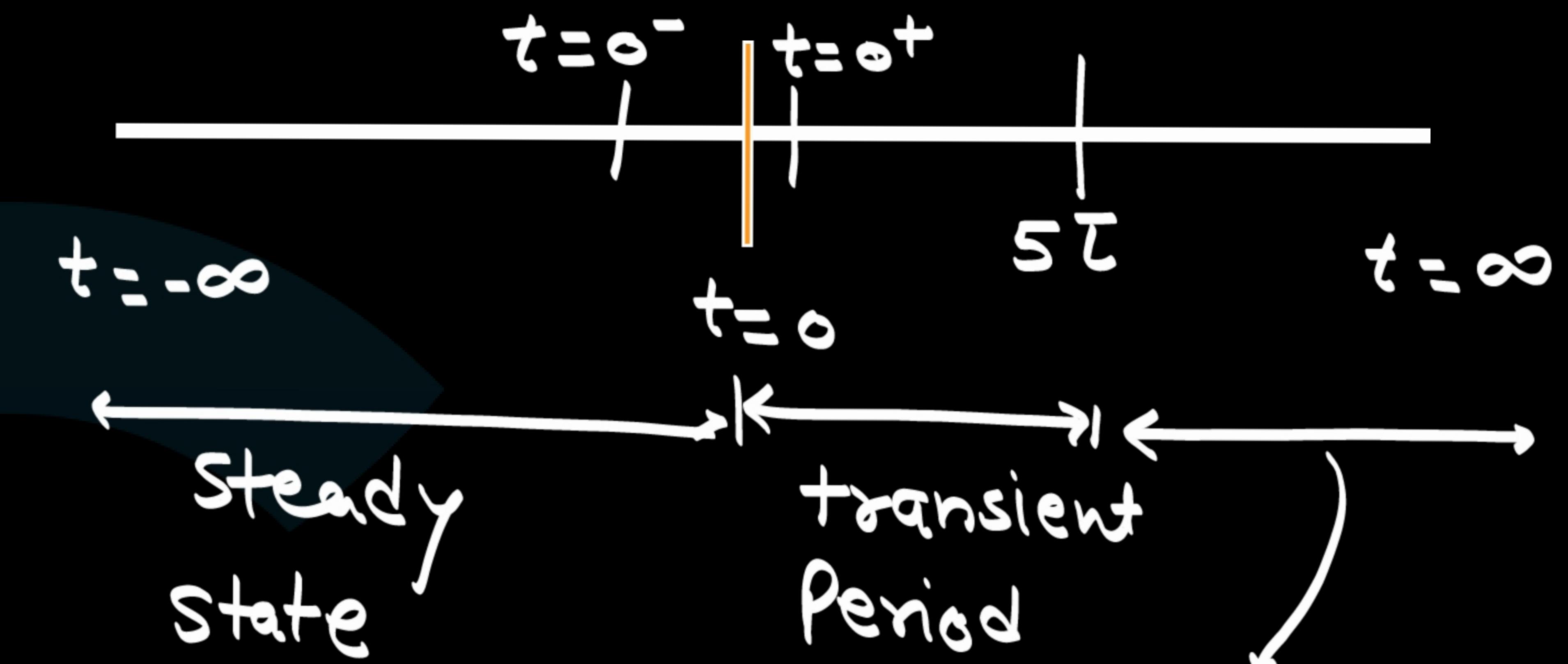Any energy storing element must present in circuit



$t=0^- \rightarrow$ time Counting initiate
 $t=0^+ \rightarrow$ just after
 $t=0^- \rightarrow$ just before.

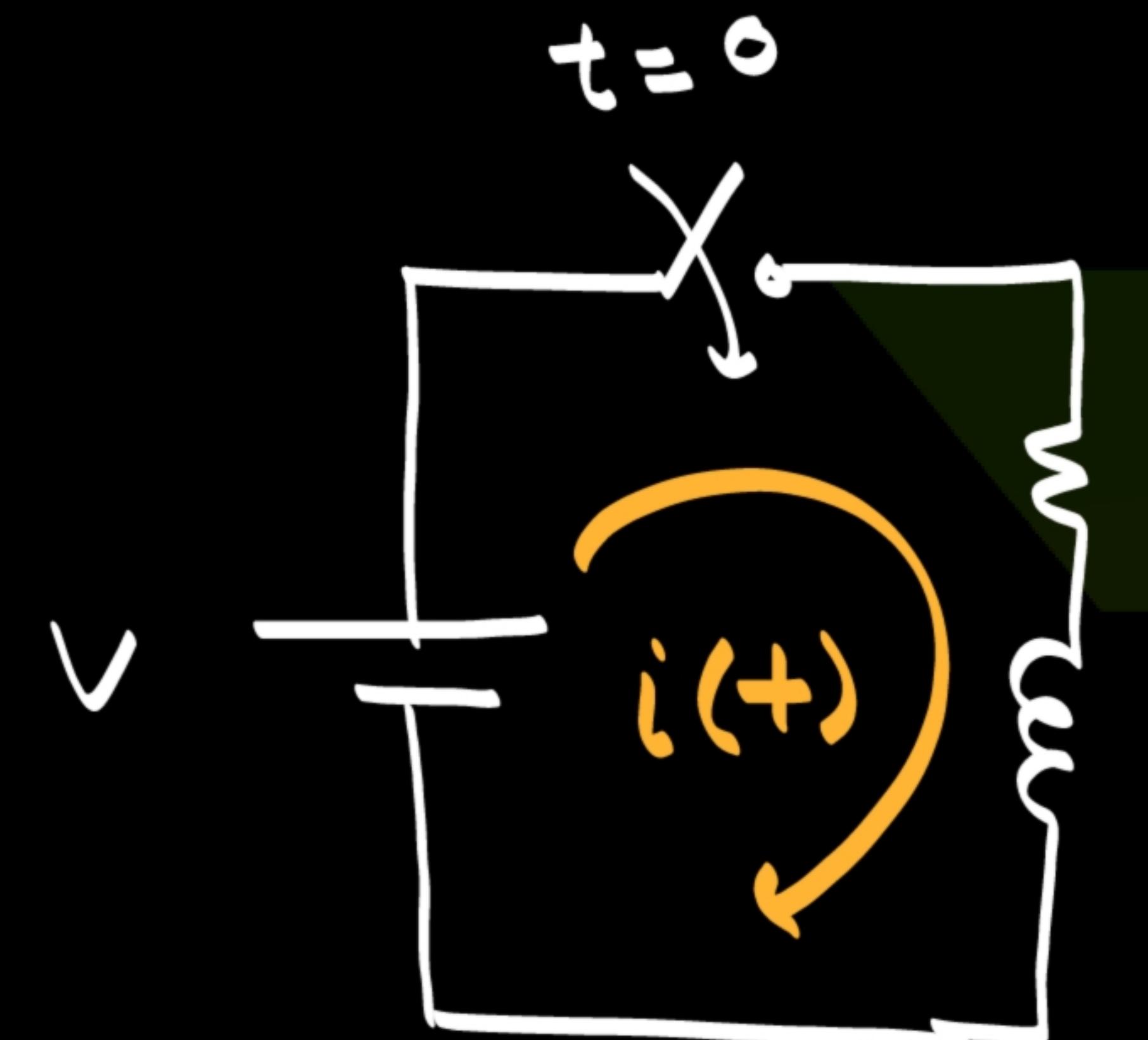Case Study
Case - I


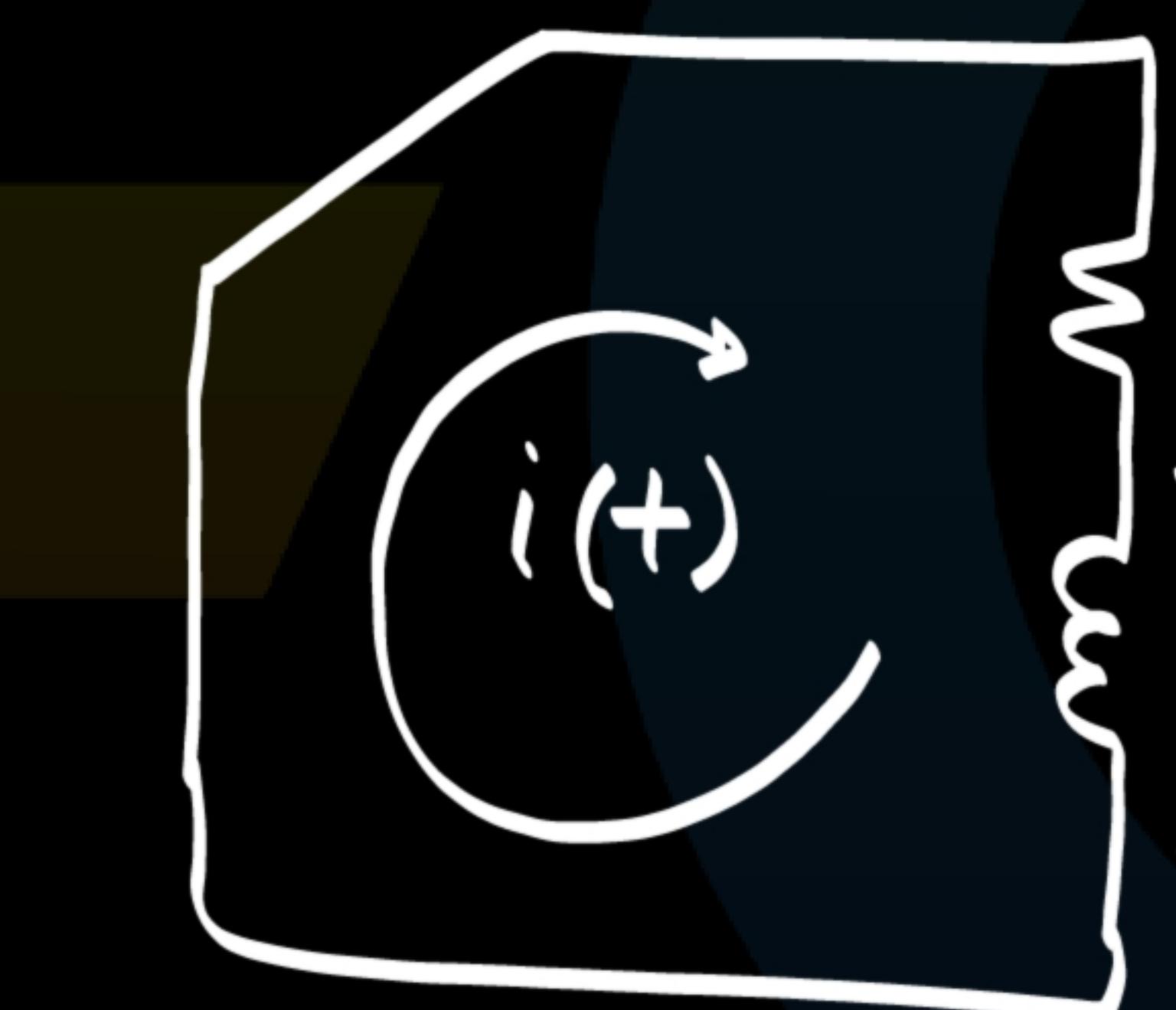
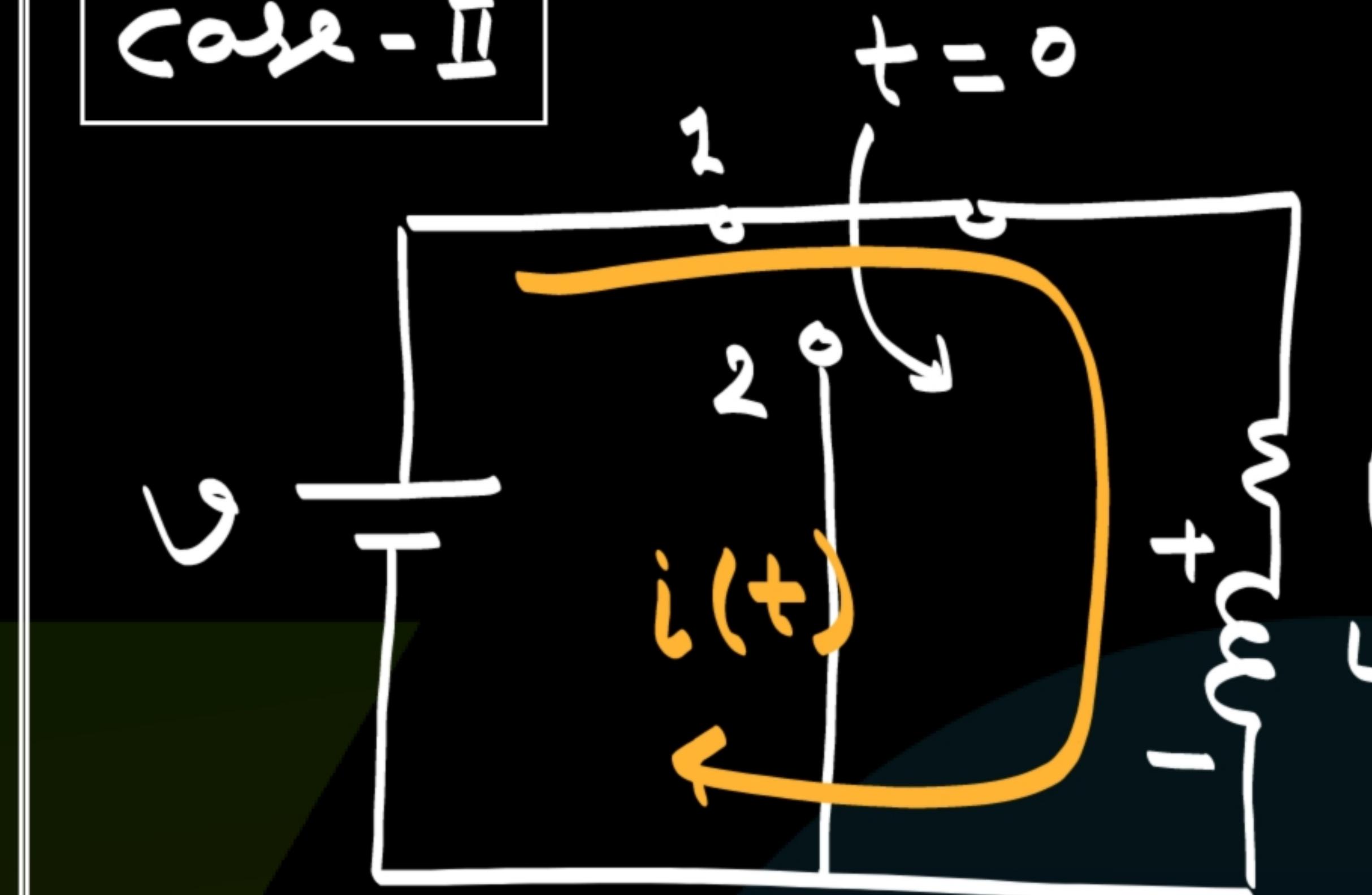
$$t = 0^-, \quad i(+)=0 \text{ Amp}$$

$$t = 0^+, \quad i(+)=0 \text{ Amp}$$

Inductor \rightarrow open circuit

$$t = \infty, \quad i(+)=\frac{V}{R} \text{ Amperes}$$


Inductor \rightarrow short circuit.

Case - II


$$t = 0^-, \quad i(+)=I_0 \quad \checkmark$$

$$t = 0^+, \quad i(t)=I_0 \quad \checkmark$$

Inductor \rightarrow Current Source
 $t = \infty, \quad i(+)=0 \text{ Amp}$ ✓

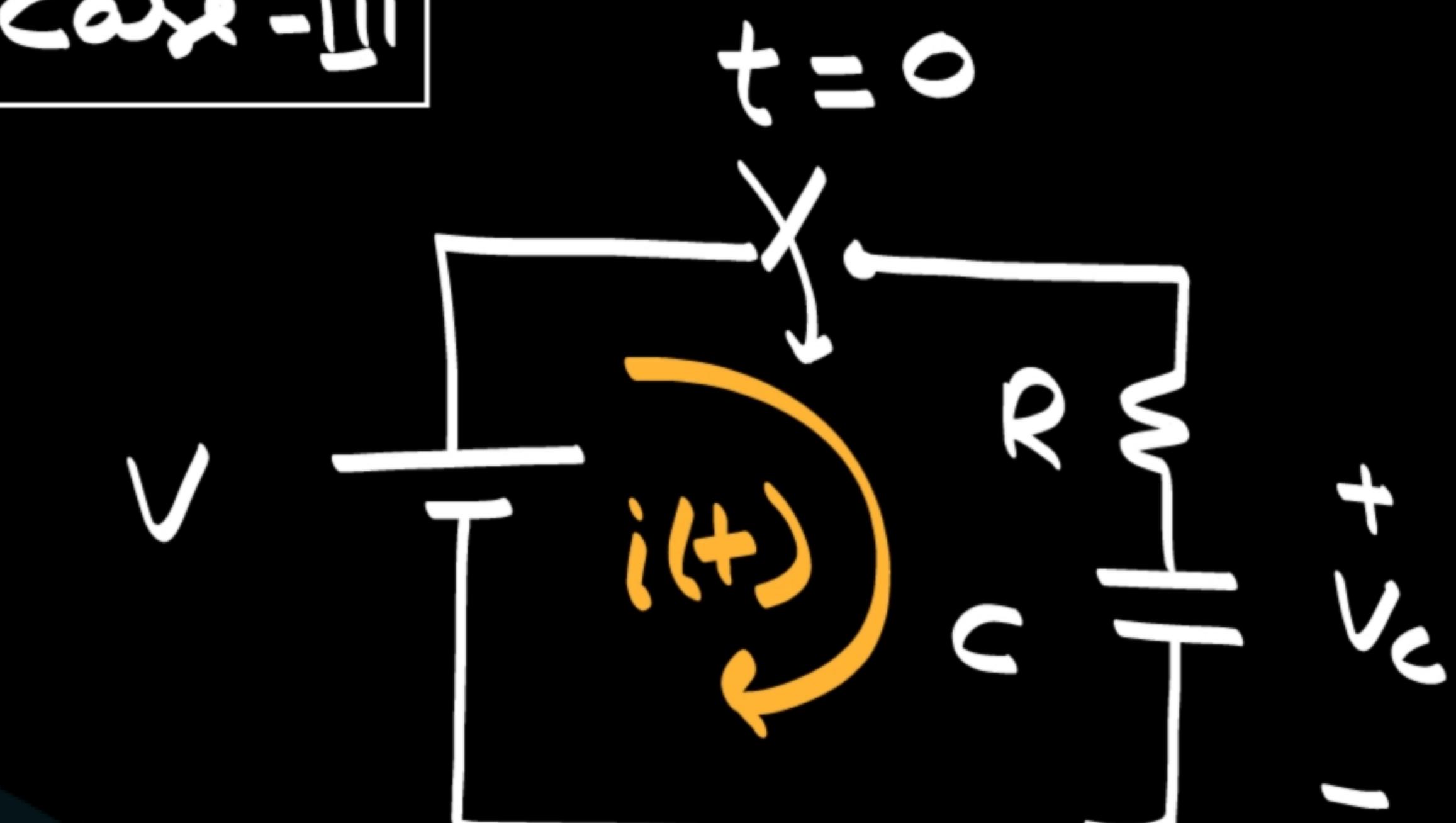Case - III


$$\text{At } t = 0^-, \quad V_C(+)=0 \text{ Volt}$$

$$\text{At } t = 0^+, \quad V_C(+)=0 \text{ Volt}$$


Capacitor \rightarrow Short Circuit.

$$\text{At } t = \infty, \quad V_C(+)=V \text{ volt}$$



$$i(+)=\frac{V-V}{R}$$

$$i(+)=0 \text{ Amp}$$

Capacitor \rightarrow Open Circuit

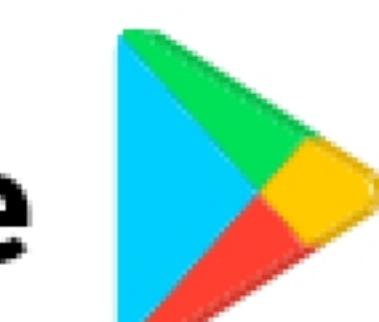

Case-IV

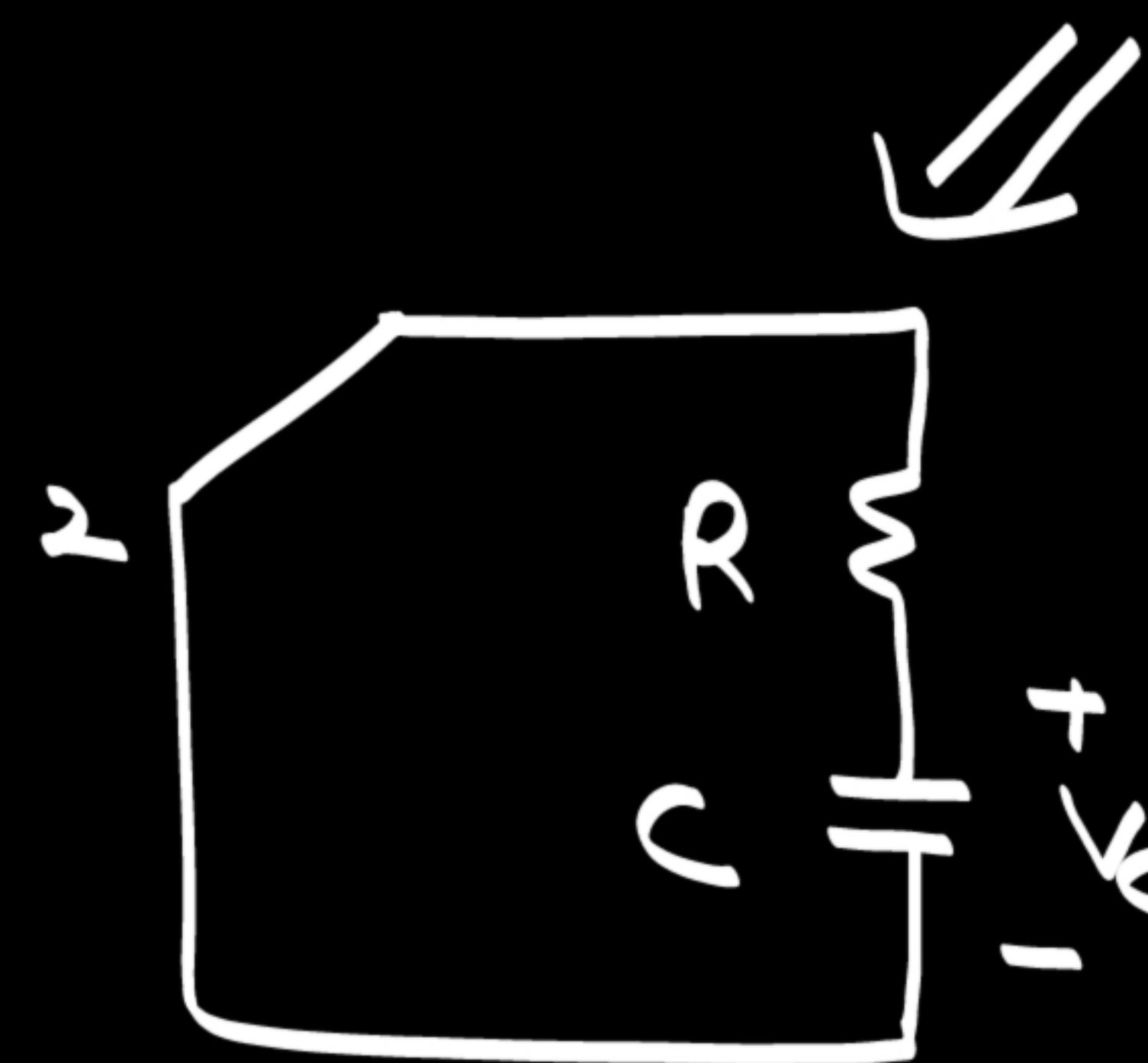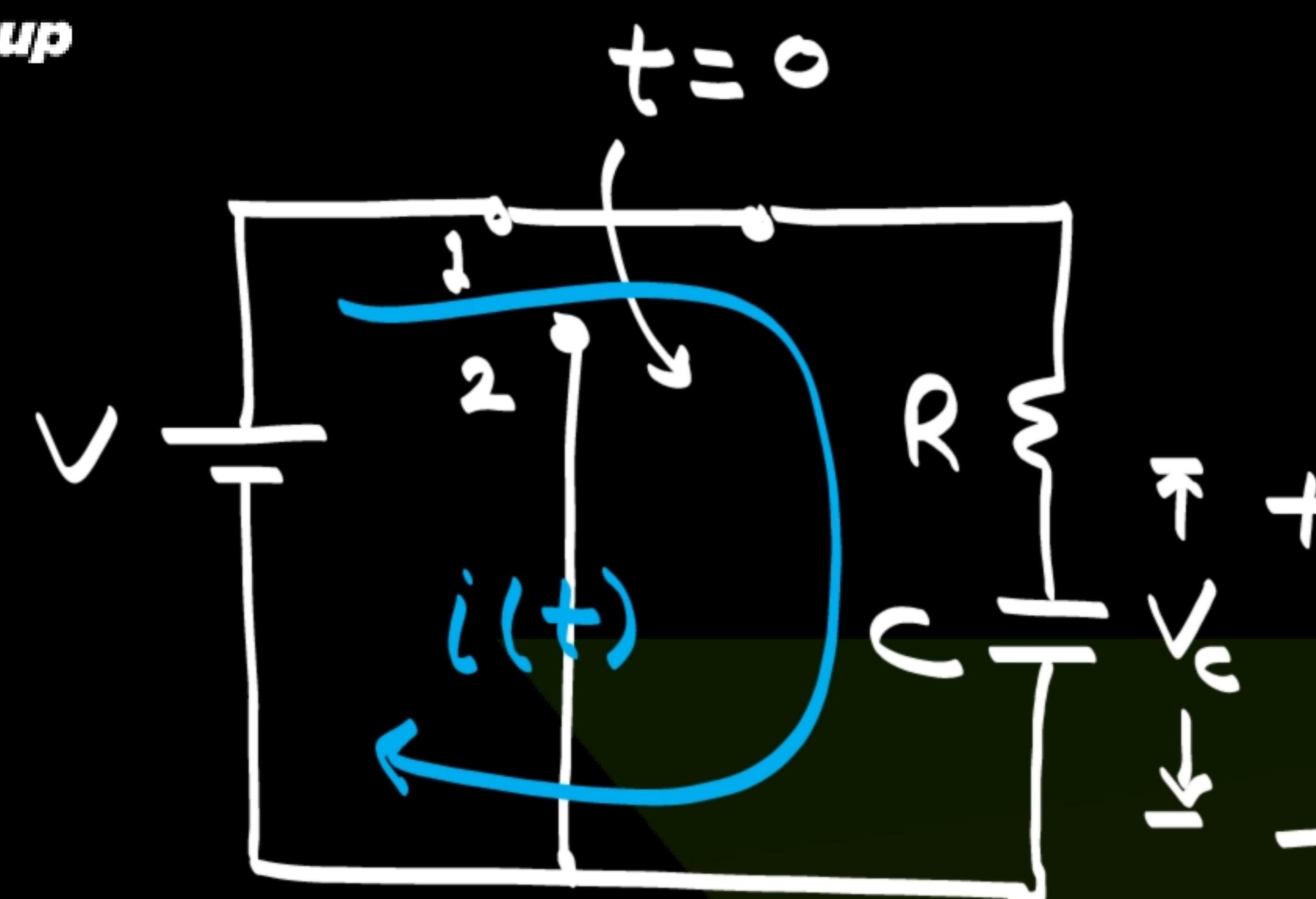

$$\text{At } t = 0^-, \quad V_c(+) = V_0 \\ \text{At } t = 0^+, \quad V_c(+) = V_0$$

Capacitor \rightarrow Voltage Source

$$t = \infty, \quad V_c(t) = 0$$


Inductor - do not accept change in current.
Capacitor - do not accept change in voltage.




Case - I

Source free RL Circuit

Discharging of
Inductor

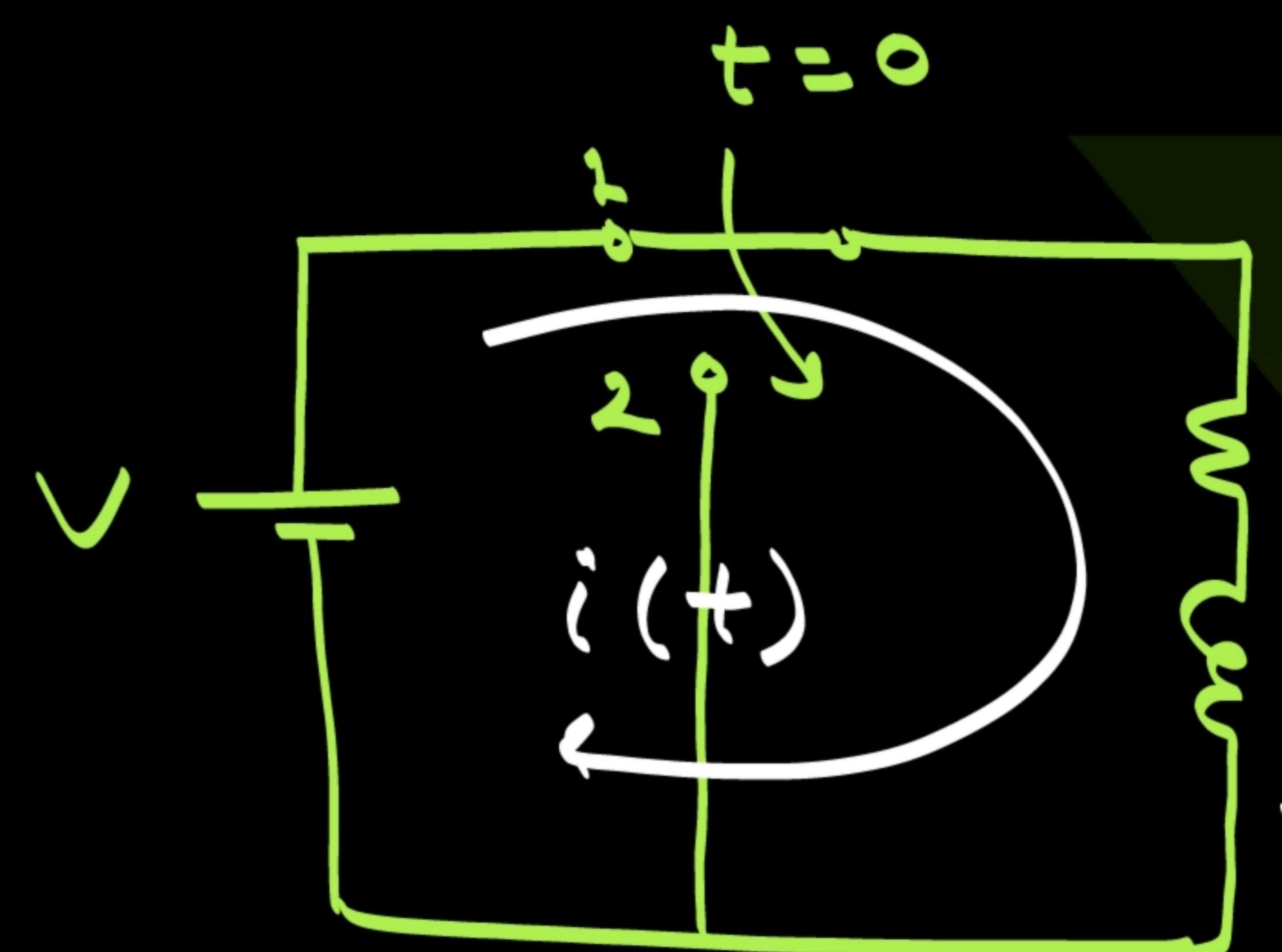
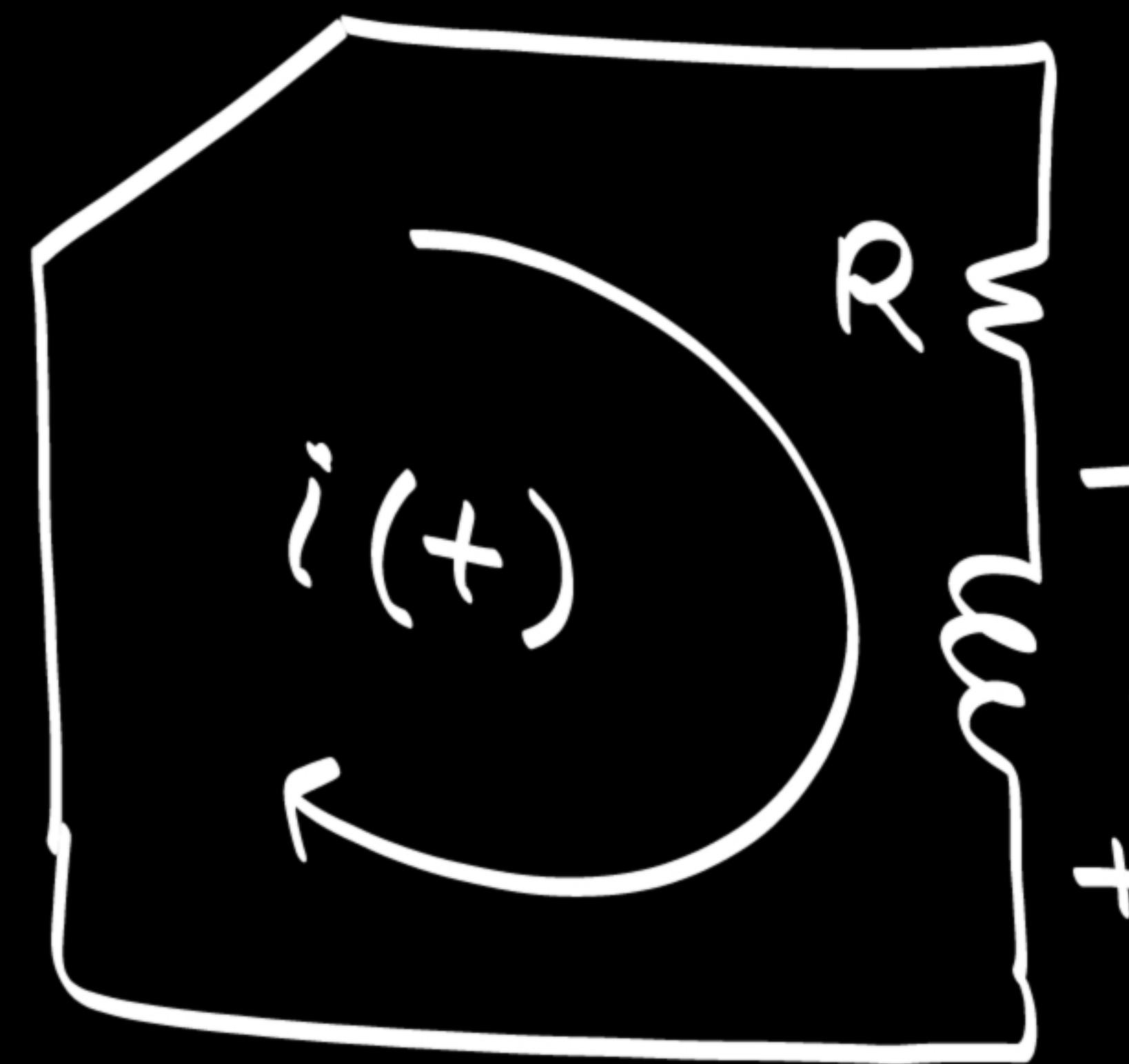
$$\begin{aligned} \text{At } t = 0^- \\ i(t) = I_0 \\ t = 0^+, \\ i(t) = I_0 \\ t = 0 \Rightarrow i(t) = I_0 \end{aligned}$$



At $t = 0$, switch is connected to Position 2 →

Apply KVL →

$$R \cdot i(t) + L \cdot \frac{di(t)}{dt} = 0$$

$$R \cdot i(t) = -L \cdot \frac{di(t)}{dt}$$

$$-\frac{R}{L} \cdot dt = \frac{di(t)}{i(t)}$$

$$\int_0^t -\frac{R}{L} \cdot dt = \int_{I_0}^{i(t)} \frac{di(t)}{i(t)}$$

$$-\frac{R}{L} \cdot t = \left[\log i(t) \right]_{I_0}^{i(t)}$$

$$-\frac{R}{L} \cdot t = \log(i(t))$$

$$-\log(I_0)$$


$$-\frac{R}{L} \cdot t = \log\left(\frac{i(t)}{I_0}\right)$$

take Antilog

$$\frac{i(t)}{I_0} = e^{-Rt/L}$$

$$i(t) = I_0 \cdot e^{-Rt/L}$$



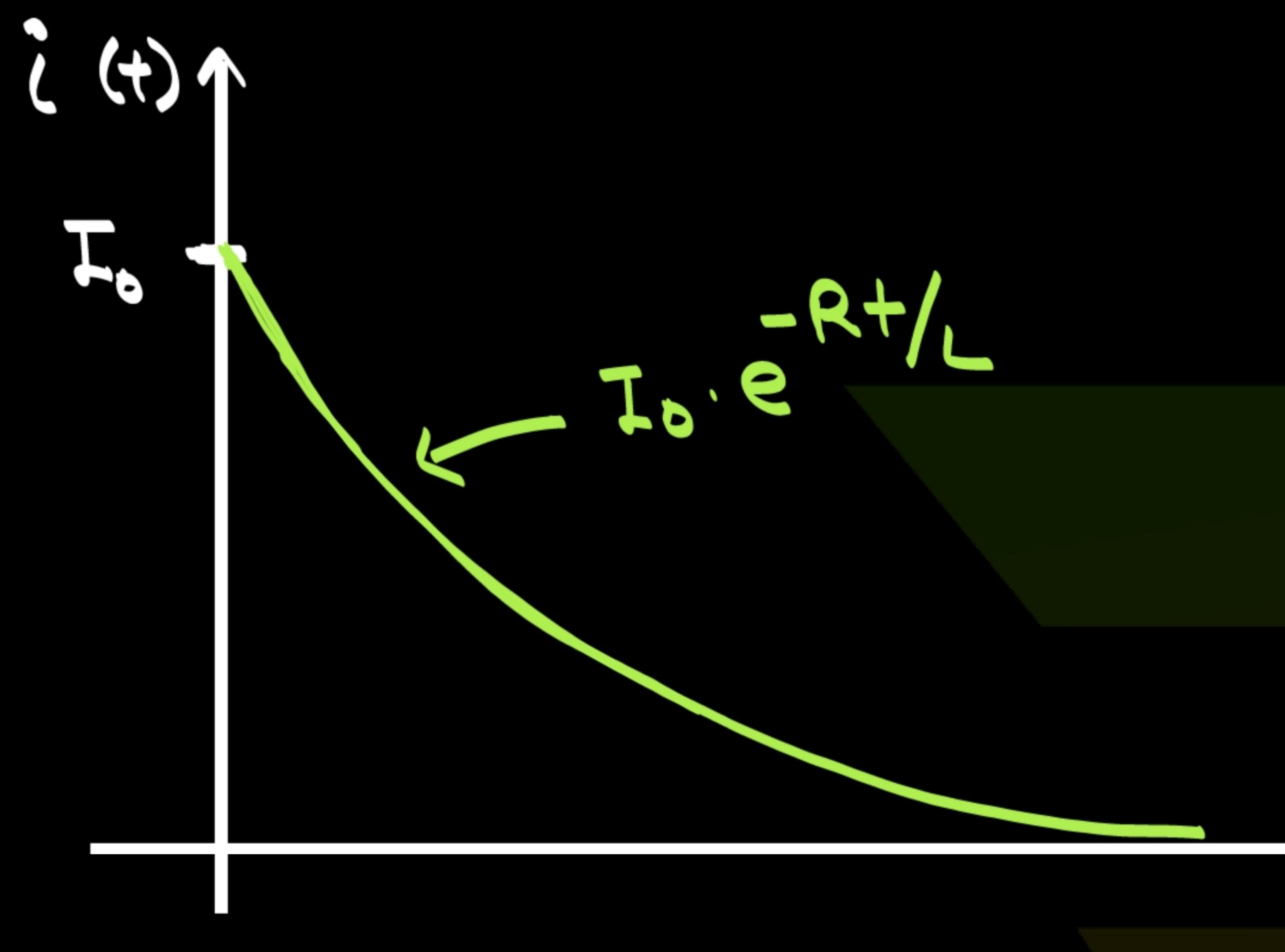

$$i(t) = I_0 \cdot e^{-Rt/L}$$

$$\text{At } t=0, \rightarrow i(t) = I_0$$

$$\text{At } t=\infty, \rightarrow i(t) = 0$$

Voltage across inductor -

$$V_L = L \cdot \frac{di(t)}{dt}$$


$$V_L = L \cdot \frac{d}{dt} I_0 \cdot e^{-Rt/L}$$

$$= I_0 \cdot L \cdot \left(-\frac{R}{L} \right) \cdot e^{-Rt/L}$$

$$V_L = -I_0 R e^{-Rt/L}$$

$$\text{let } (V_0 = I_0 R)$$

$$V_L = -V_0 \cdot e^{-Rt/L}$$

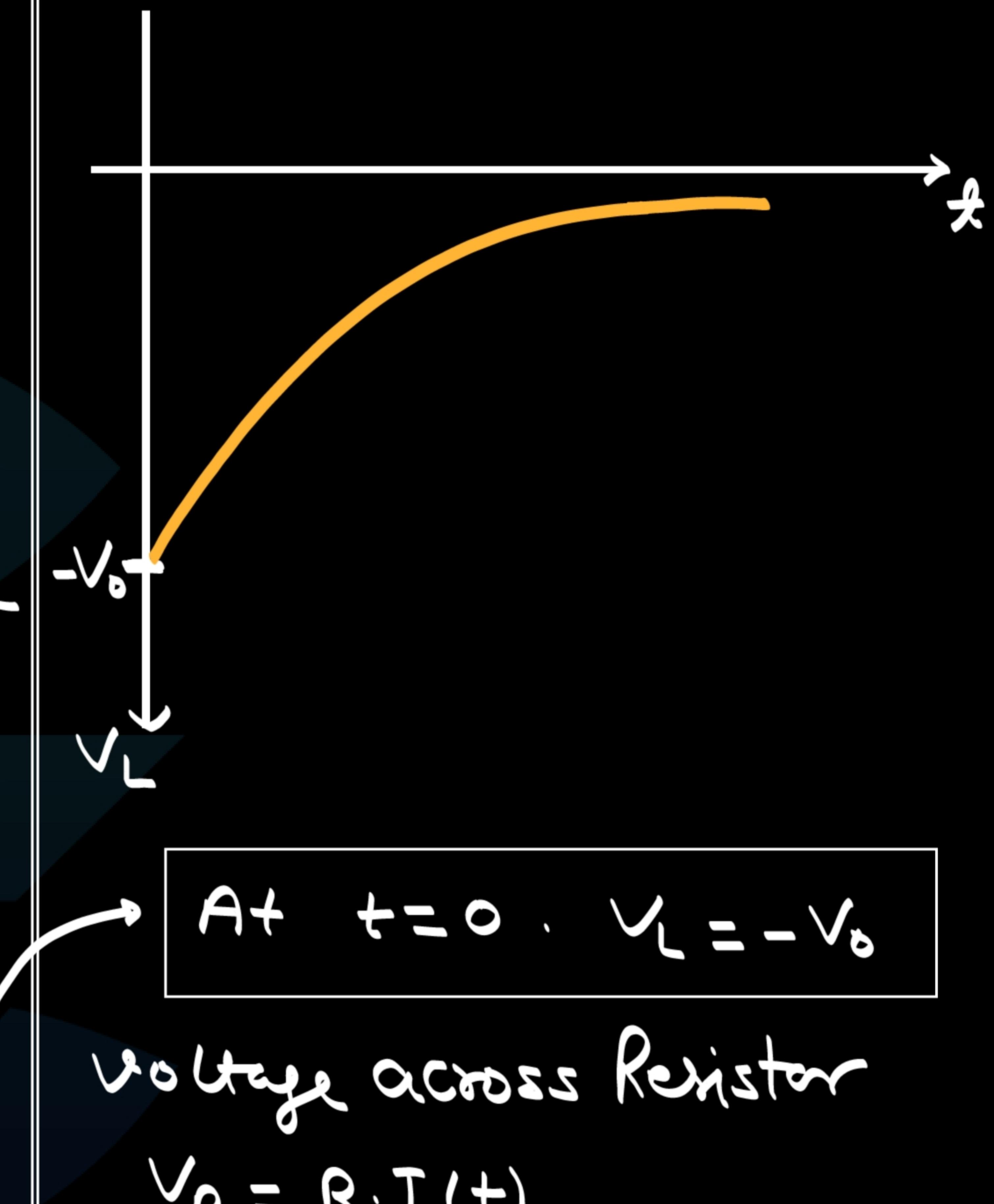


$$V_R = R \cdot I(t)$$

$$= R \cdot I_0 \cdot e^{-Rt/L}$$

$$V_R = V_0 \cdot e^{-Rt/L}$$




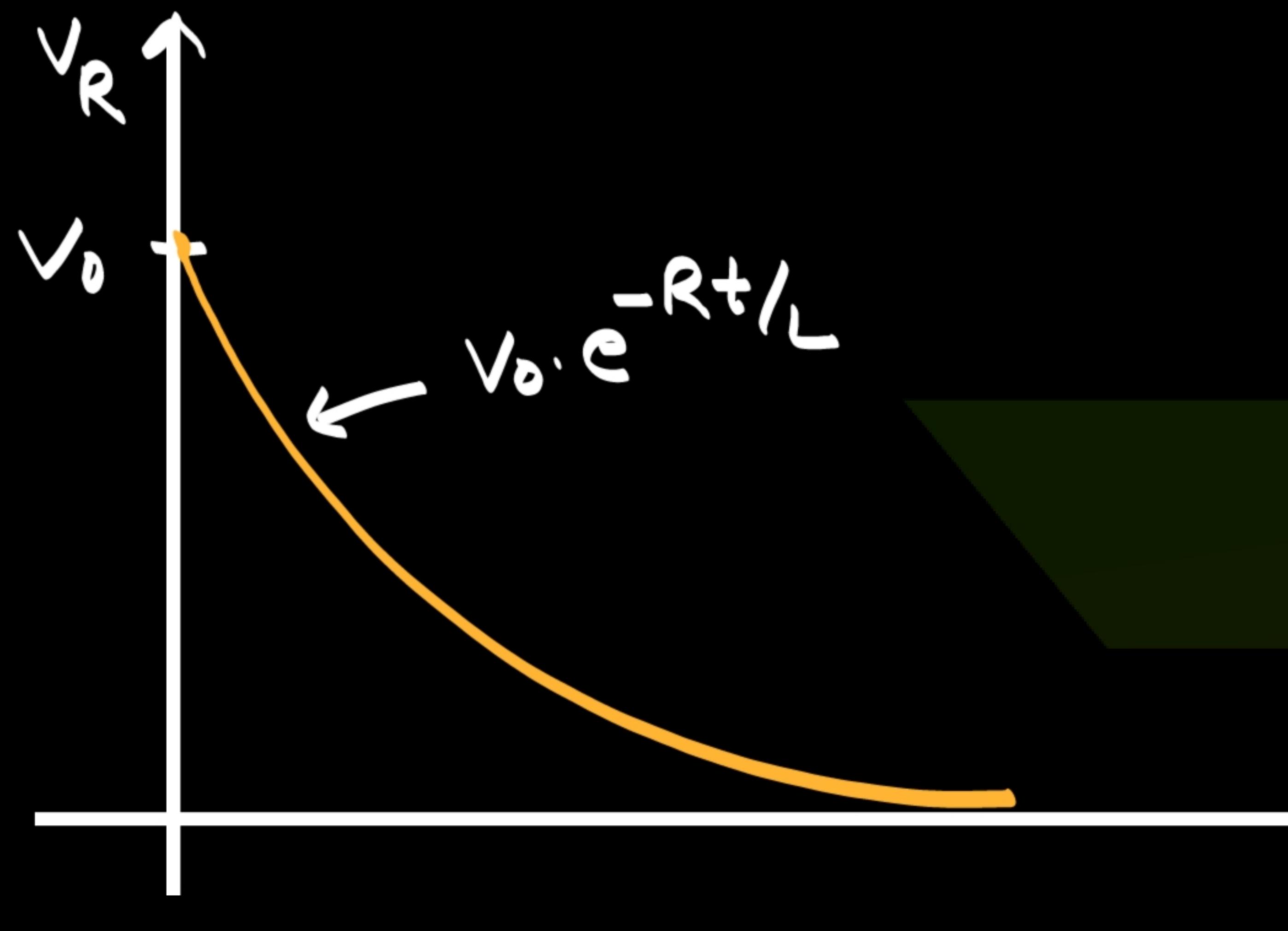

Case-II

RL Circuit with Source

Charging

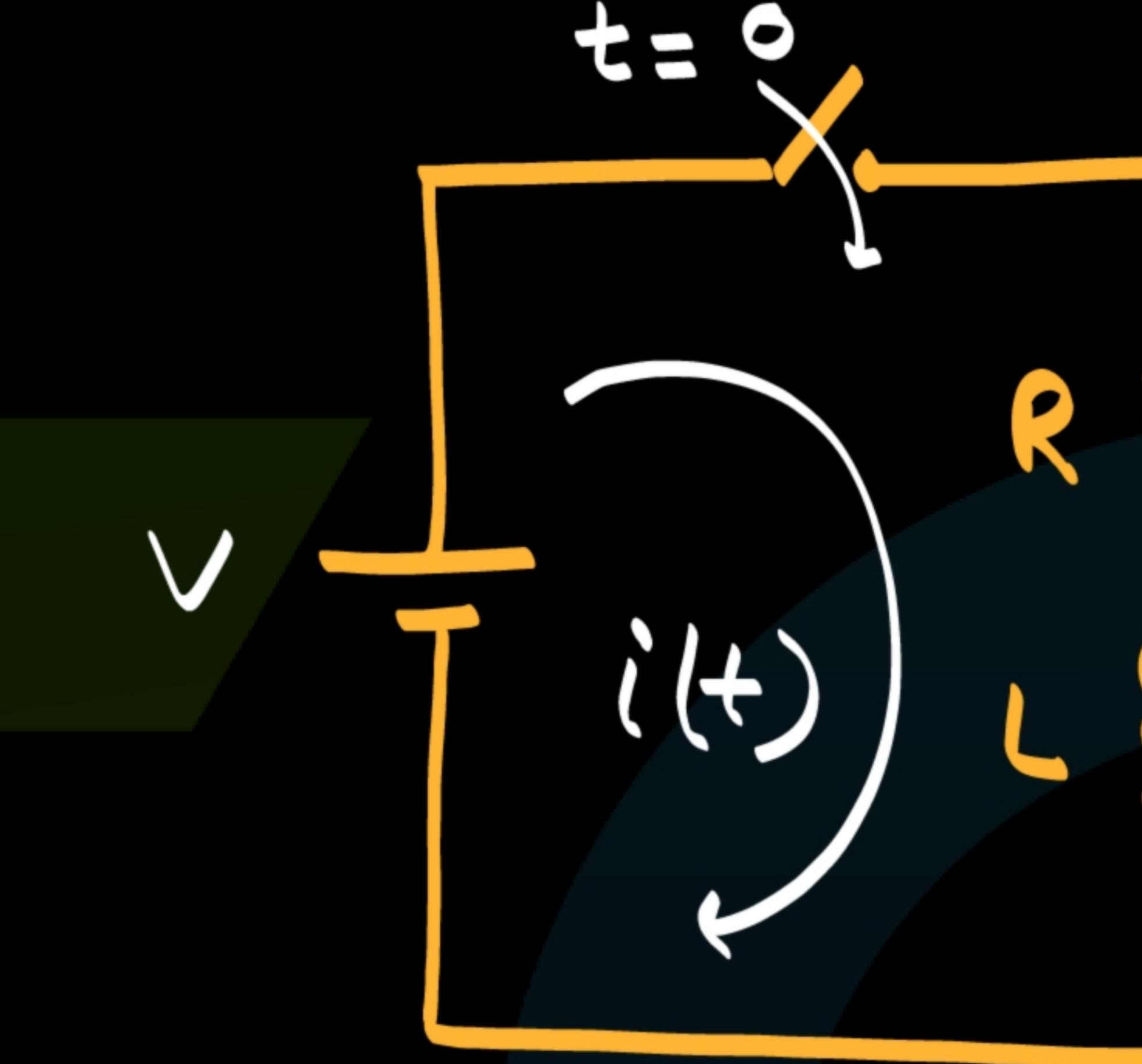

At $t=0 \rightarrow$ switch will Connect.

Apply KVL \rightarrow

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

Divide above eqn with $L \rightarrow$

$$\frac{V}{L} = \frac{R}{L} \cdot i + \frac{1}{L} \cdot \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} \cdot i = \frac{V}{L}$$

$$i(t) = C.F. + P.I.$$

transient

steady state



C.F. \rightarrow transient response \rightarrow

$$\frac{di}{dt} + \frac{R}{L} \cdot i = 0$$

After solving this.

$$i(t) = A \cdot e^{-Rt/L} \rightarrow \textcircled{I}$$

$A \rightarrow$ Constant

P.I. \rightarrow steady state

$$i(t) = \frac{V}{R} \rightarrow \textcircled{II}$$

$$i(t) = C.F. + P.I.$$

$$i(t) = A \cdot e^{-Rt/L} + \frac{V}{R}$$

$$\text{At } t = 0^-, i(t) = 0$$

$$t = 0^+, i(t) = 0$$

$$t = \infty, i(t) = 0$$

$$\text{So, } 0 = A \cdot e^0 + \frac{V}{R}$$

$$e^0 = 1$$

$$0 - \frac{V}{R} = A$$

$$i(\infty) = \frac{V}{R}$$

$$A = i(0^+) - i(\infty)$$

so,

$$i(t) = \left\{ i(0^+) - i(\infty) \right\} e^{-\frac{Rt}{L}} + \frac{V}{R}$$

$$i(t) = \left(i(0^+) - i(\infty) \right) e^{-\frac{Rt}{L}} + i(\infty)$$


$$i(t) = \left(0 - \frac{V}{R} \right) e^{-\frac{Rt}{L}} + \frac{V}{R}$$

$$i(t) = \frac{V}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

$$\text{Let } I_0 = \frac{V}{R}$$
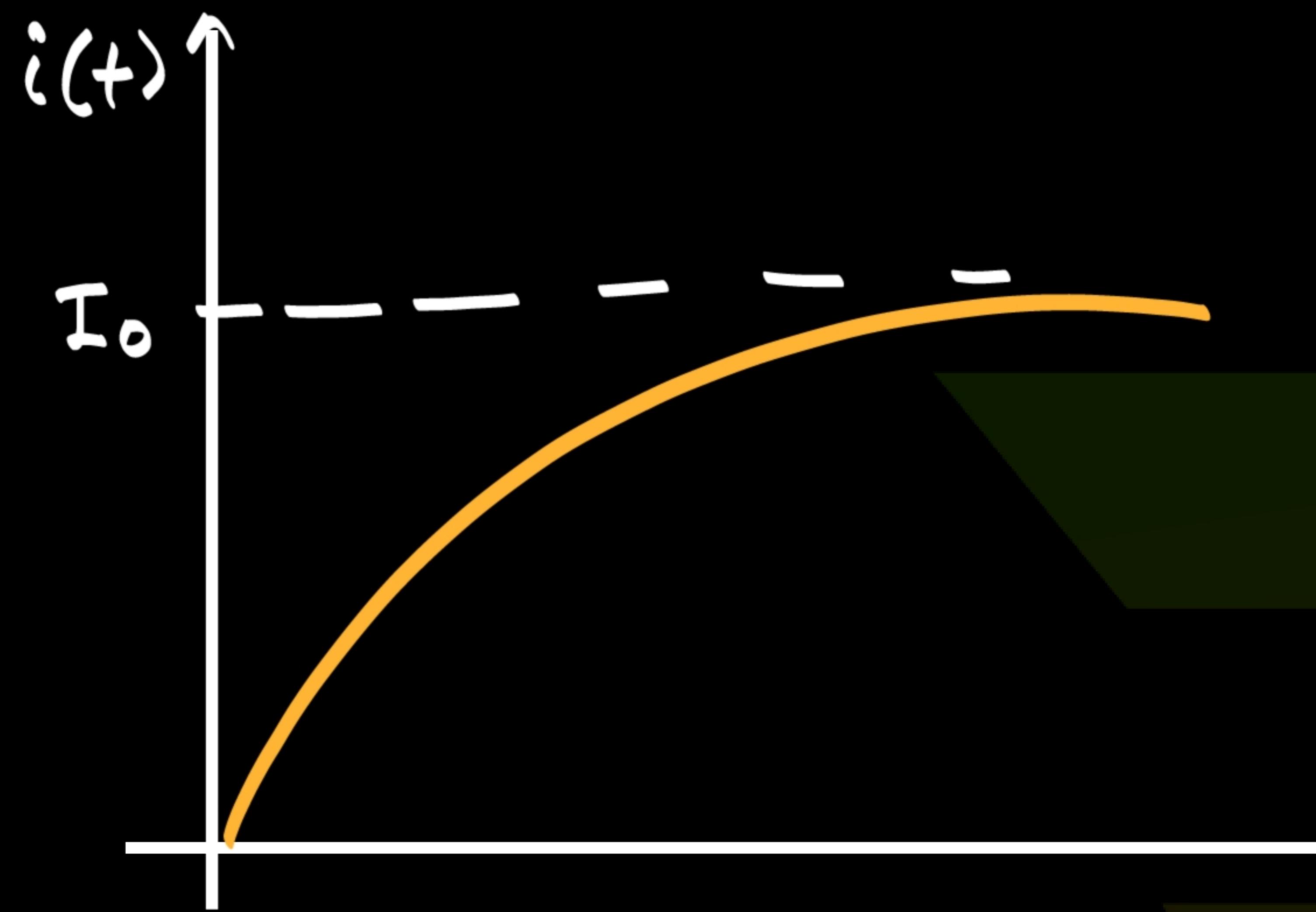
$$i(t) = I_0 \left(1 - e^{-\frac{Rt}{L}} \right)$$





$$i(t) = I_0(1 - e^{-Rt/L})$$

 $\tau = \infty$


$$i(t) = I_0$$

Voltage across Resistor.

$$V_R = R \cdot i(t)$$

$$V_R = R \cdot I_0 \cdot (1 - e^{-Rt/L})$$

$$V_R = V_0 \cdot (1 - e^{-Rt/L})$$

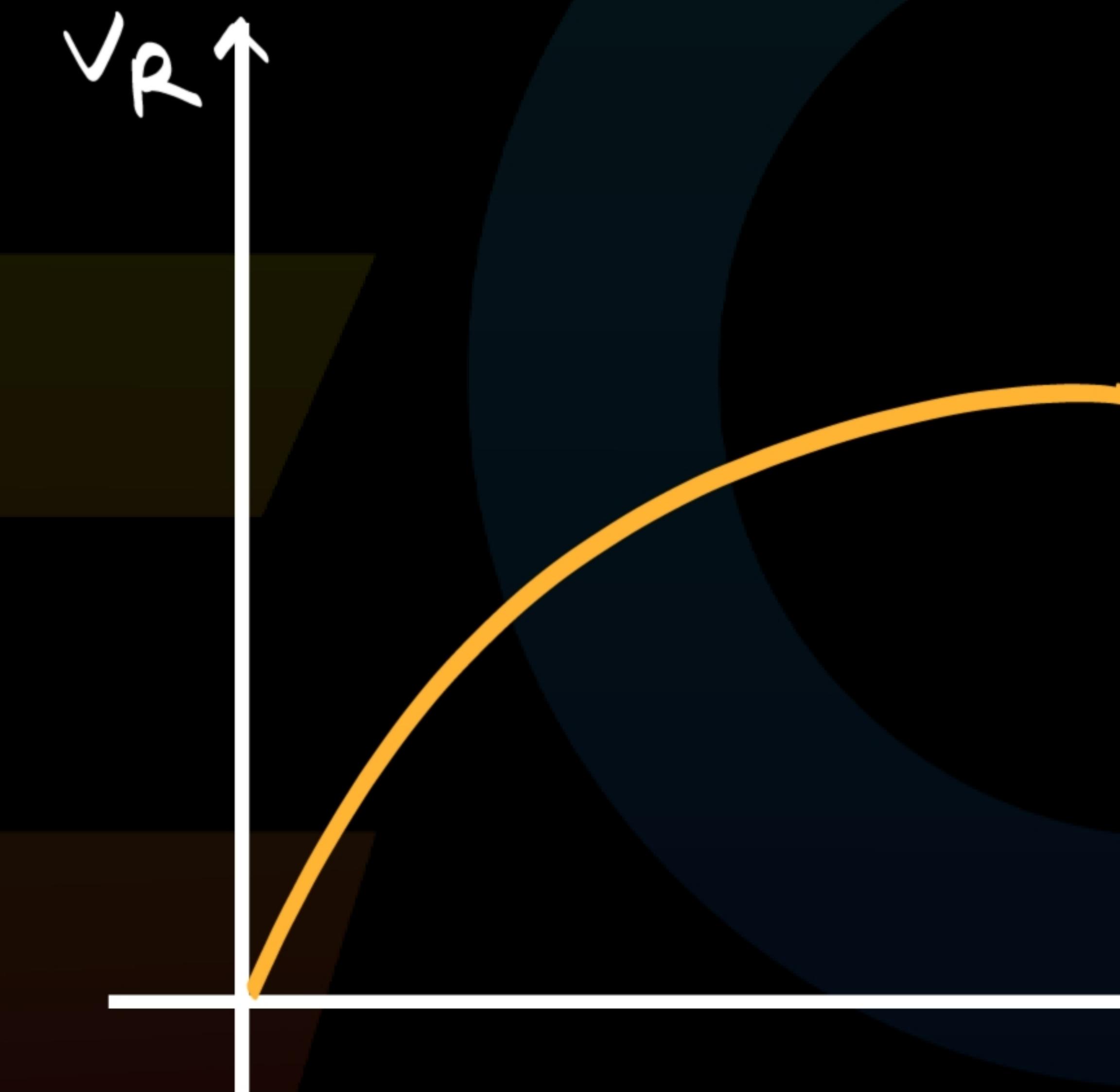 V_R
 t


Voltage across inductor.

$$V_L = L \cdot \frac{di(t)}{dt}$$

$$V_L = L \cdot \frac{d}{dt} I_0 (1 - e^{-Rt/L})$$

$$V_L = L \cdot I_0 \left(0 + \frac{R}{L} \cdot e^{-Rt/L} \right)$$

$$V_L = I_0 \cdot R \cdot e^{-Rt/L}$$

$$V_L = V_0 \cdot e^{-Rt/L}$$

$$V_0 = I_0 \cdot R$$

