

लक्ष्य बैच

ELECTRICAL ENGINEERING

KEY FEATURES:-

- + Live & recorded classes:
- + Class notes in PDF Form
- + Doubt Sessions
- + Practice sessions
- + Test series

Download EAD Online Classes on Playstore

ENROLL NOW



AE | ASSISTANT ENGINEER

exam targeted:-

UPPCL AE, UPPSC, AE, UKPSC AE,
MAHATRANSCO AE AND
OTHER STATE AE / PSU EXAMS



--EAD EXPERTS



for more information contact us:-

8126989696, 7505771800, 8449597123, 8057871234



EAD ONLINE CLASSES


DC transients

Transients present in any circuit due to change in source magnitude or load elements, and it contains energy storing elements.

Energy storing Element \rightarrow Inductor \rightarrow mag. form
Capacitor \rightarrow Electrostatic form.

In Pure resistive circuit \rightarrow Transients are not present.

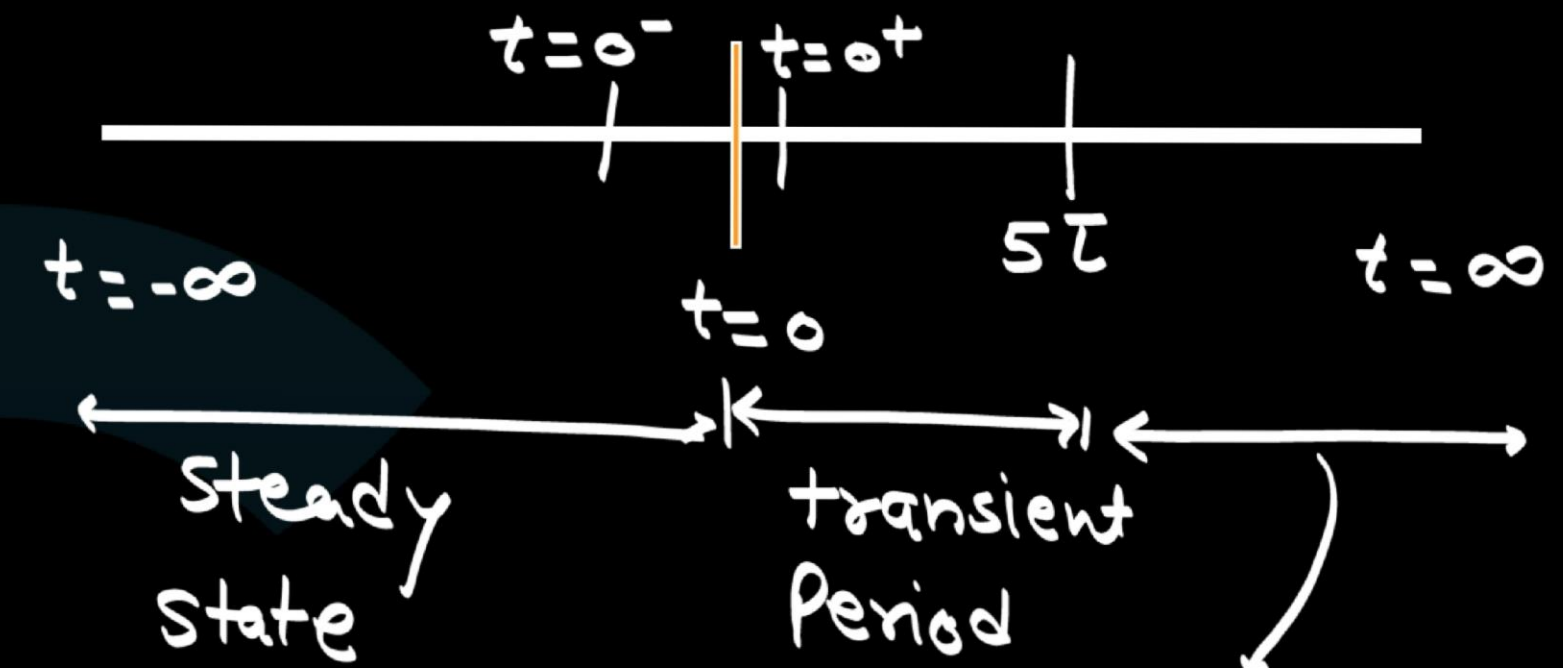Any energy storing element must present in circuit




$t = 0 \rightarrow$ time counting initiate
 $t = 0^+ \rightarrow$ just after
 $t = 0^- \rightarrow$ just before.

steady state



Case study

Case - I

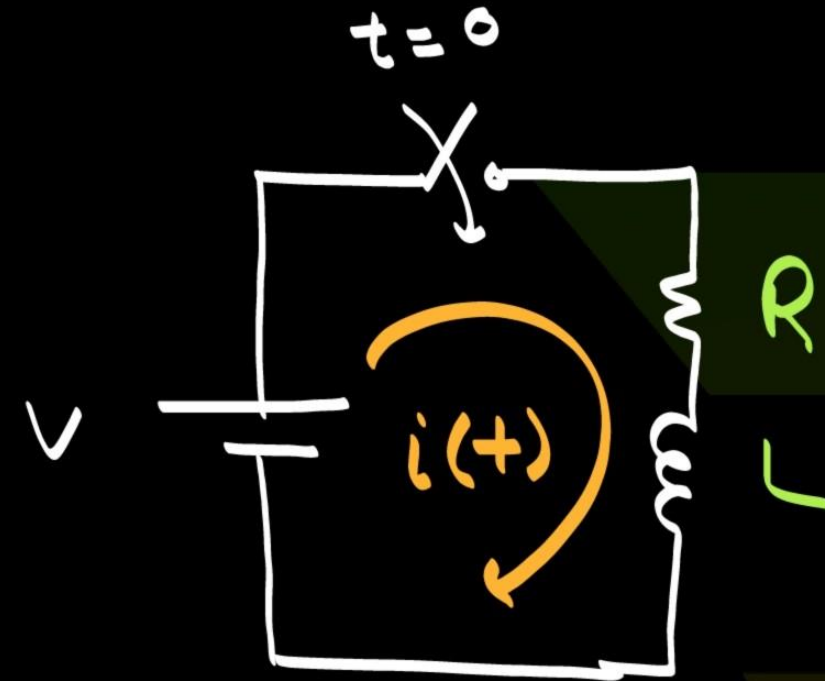

$$t=0^-, i(t) = 0 \text{ Amp}$$



$$t=0^+, i(t) = 0 \text{ Amp}$$

Inductor \rightarrow open circuit

$$t=\infty, i(t) = \frac{V}{R} \text{ Ampere}$$

Inductor \rightarrow short circuit.

Case - II

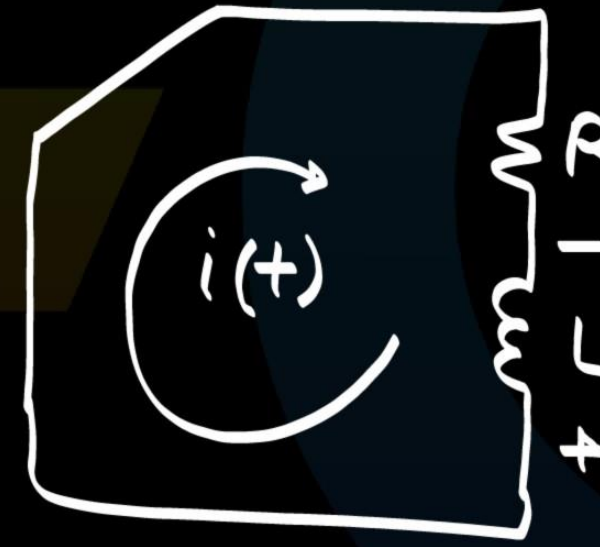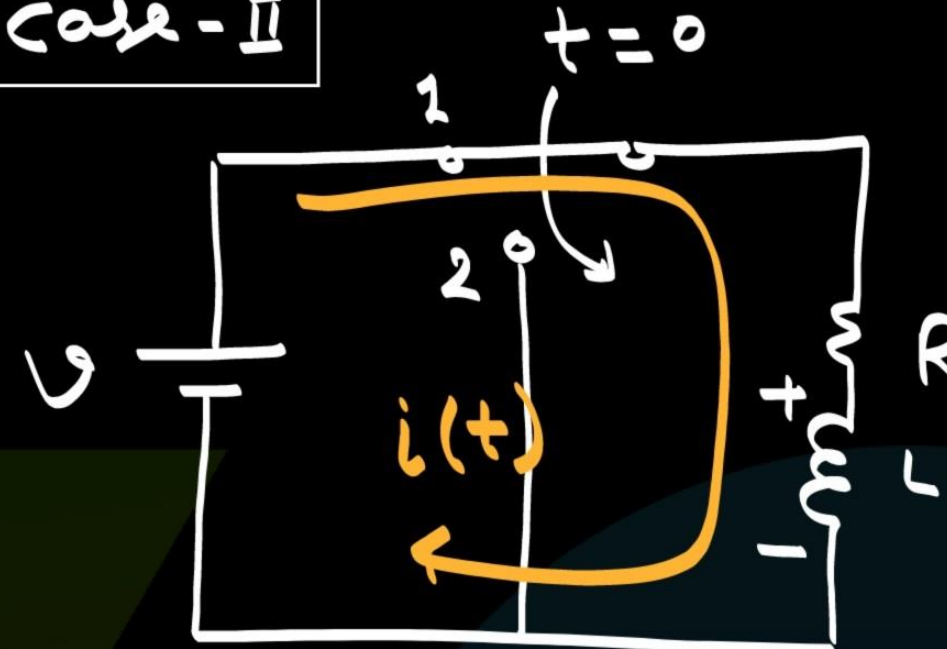


$$t=0^-, i(t) = I_0 \checkmark$$

$$t=0^+, i(t) = I_0 \checkmark$$

Inductor \rightarrow Current Source

$$t=\infty, i(t) = 0 \text{ Amp} \checkmark$$

Case - III

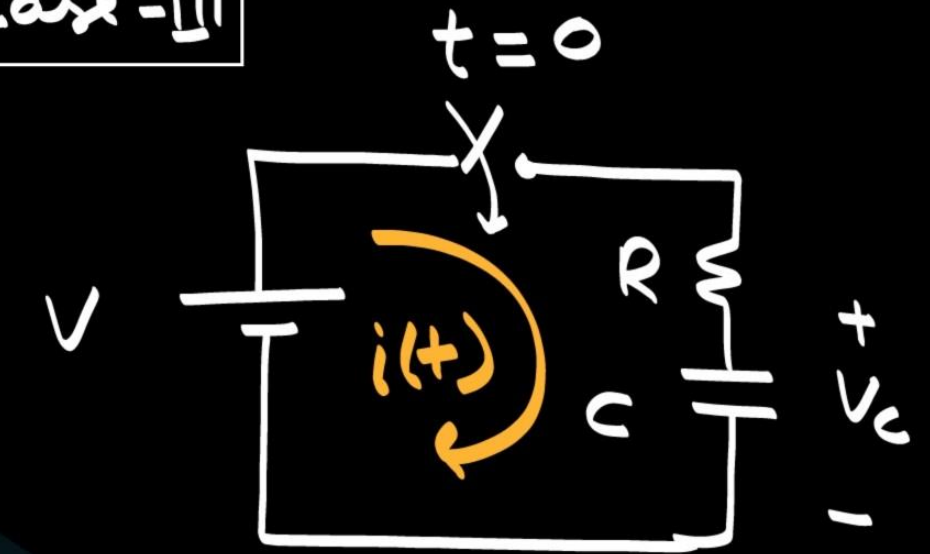

$$\text{At } t=0^-, V_c(t) = 0 \text{ Volt}$$

$$\text{At } t=0^+, V_c(t) = 0 \text{ Volt}$$

Capacitor \rightarrow short Circuit.

$$\text{At } t=\infty, V_c(t) = V \text{ Volt}$$



$$i(t) = \frac{V-V}{R}$$

$$i(t) = 0 \text{ Amp}$$

Capacitor \rightarrow open Circuit



Case-IV

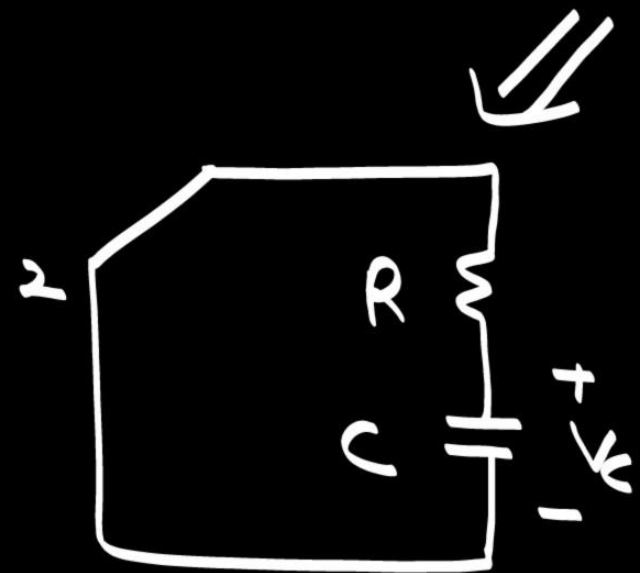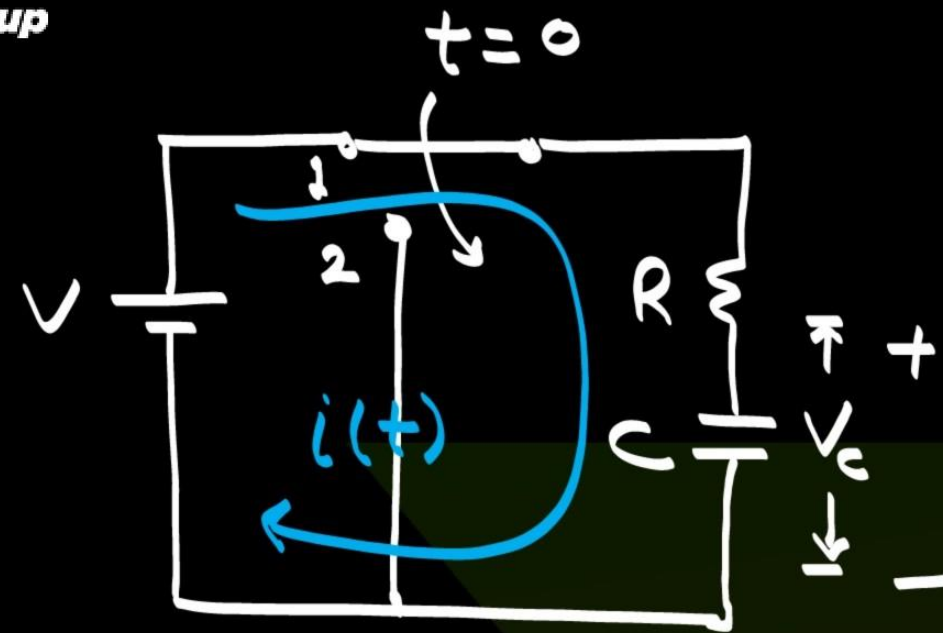

At $t = 0^-$, $V_c(t) = V_0$

$t = 0^+$, $V_c(t) = V_0$

Capacitor \rightarrow Voltage Source

$t = \infty$, $V_c(t) = 0$

Inductor - do not accept change in current.


Capacitor - do not accept change in voltage.




Case - I

Source free RL Circuit

Discharging of Inductor

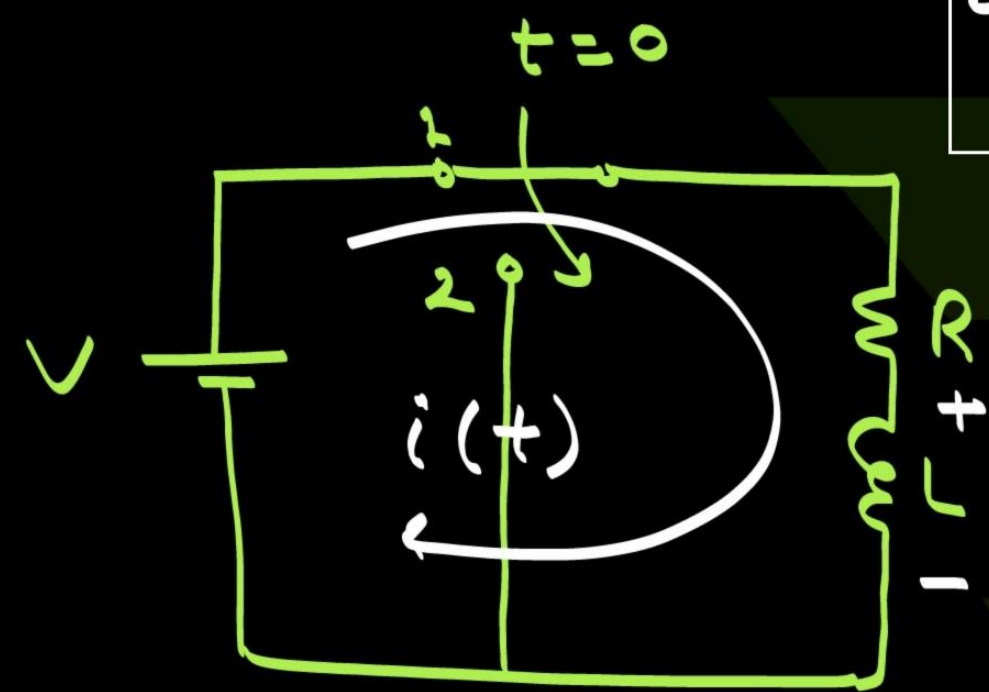

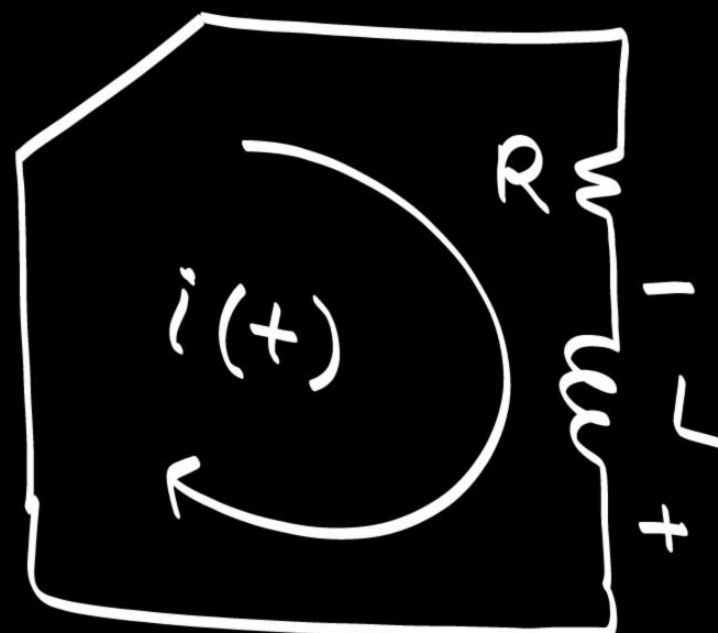At $t = 0^-$
 $i(t) = I_0$
 $t = 0^+$
 $i(t) = I_0$
 $t = 0 \rightarrow i(t) = I_0$



At $t = 0$, switch is connected to Position 2 \rightarrow
Apply KVL \rightarrow

$$R \cdot i(t) + L \cdot \frac{di(t)}{dt} = 0$$

$$R \cdot i(t) = -L \cdot \frac{di(t)}{dt}$$

$$-\frac{R}{L} \cdot dt = \frac{di(t)}{i(t)}$$

$$\int_0^t -\frac{R}{L} \cdot dt = \int_{I_0}^{i(t)} \frac{di(t)}{i(t)}$$

$$-\frac{R}{L} \cdot t = \left[\log i(t) \right]_{I_0}^{i(t)}$$

$$-\frac{R}{L} \cdot t = \log(i(t)) - \log(I_0)$$


$$-\frac{R}{L} \cdot t = \log\left(\frac{i(t)}{I_0}\right)$$

take Antilog

$$\frac{i(t)}{I_0} = e^{-Rt/L}$$

$$i(t) = I_0 \cdot e^{-Rt/L}$$



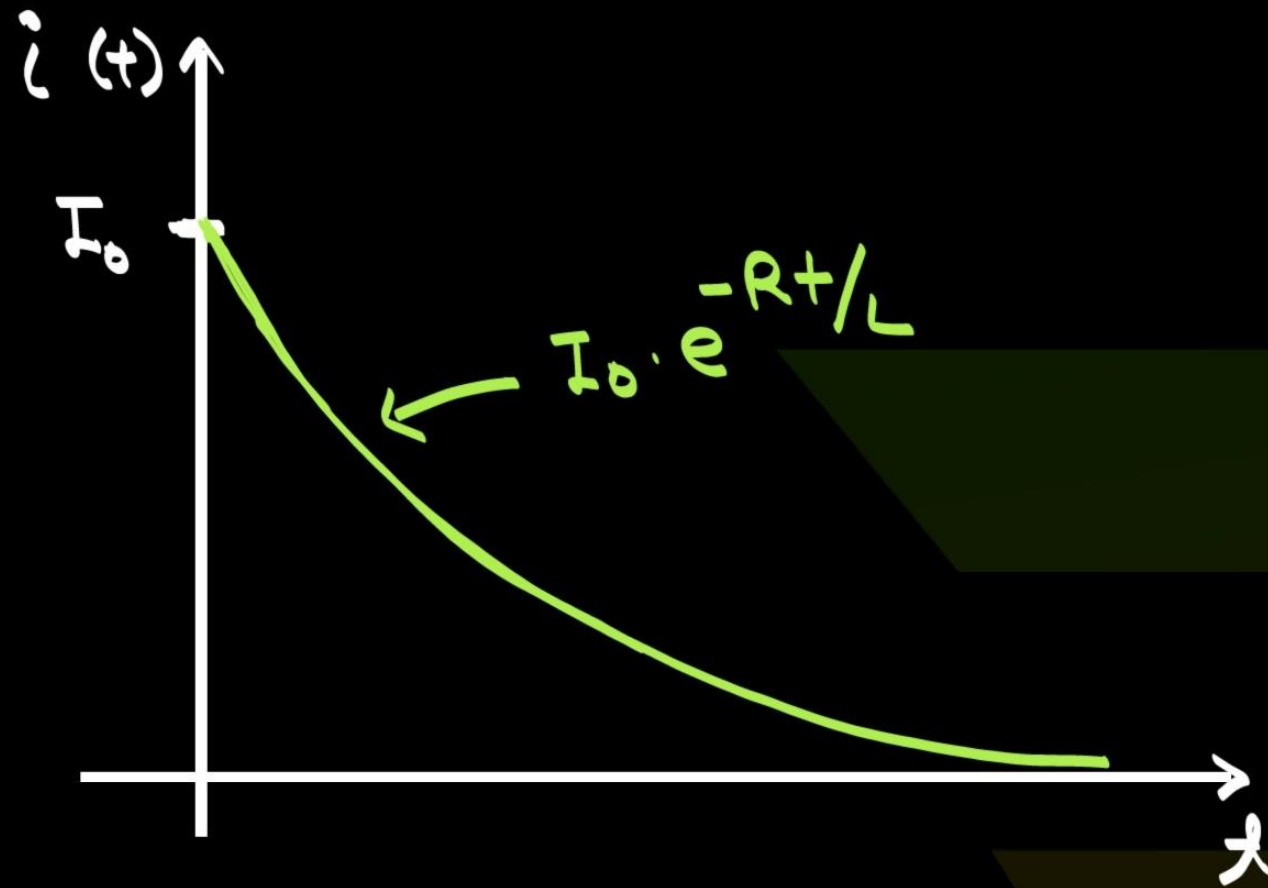

$$i(t) = I_0 \cdot e^{-Rt/L}$$

At $t=0$, $\rightarrow i(t) = I_0$

At $t=\infty$, $\rightarrow i(t) = 0$

voltage across inductor -

$$V_L = L \cdot \frac{di(t)}{dt}$$


$$V_L = L \cdot \frac{d}{dt} I_0 \cdot e^{-Rt/L}$$

$$= I_0 \cdot \cancel{L} \cdot \left(-\frac{R}{\cancel{L}} \right) \cdot e^{-Rt/L}$$

$$V_L = -I_0 R e^{-Rt/L}$$

let $(V_0 = I_0 R)$

$$V_L = -V_0 \cdot e^{-Rt/L}$$

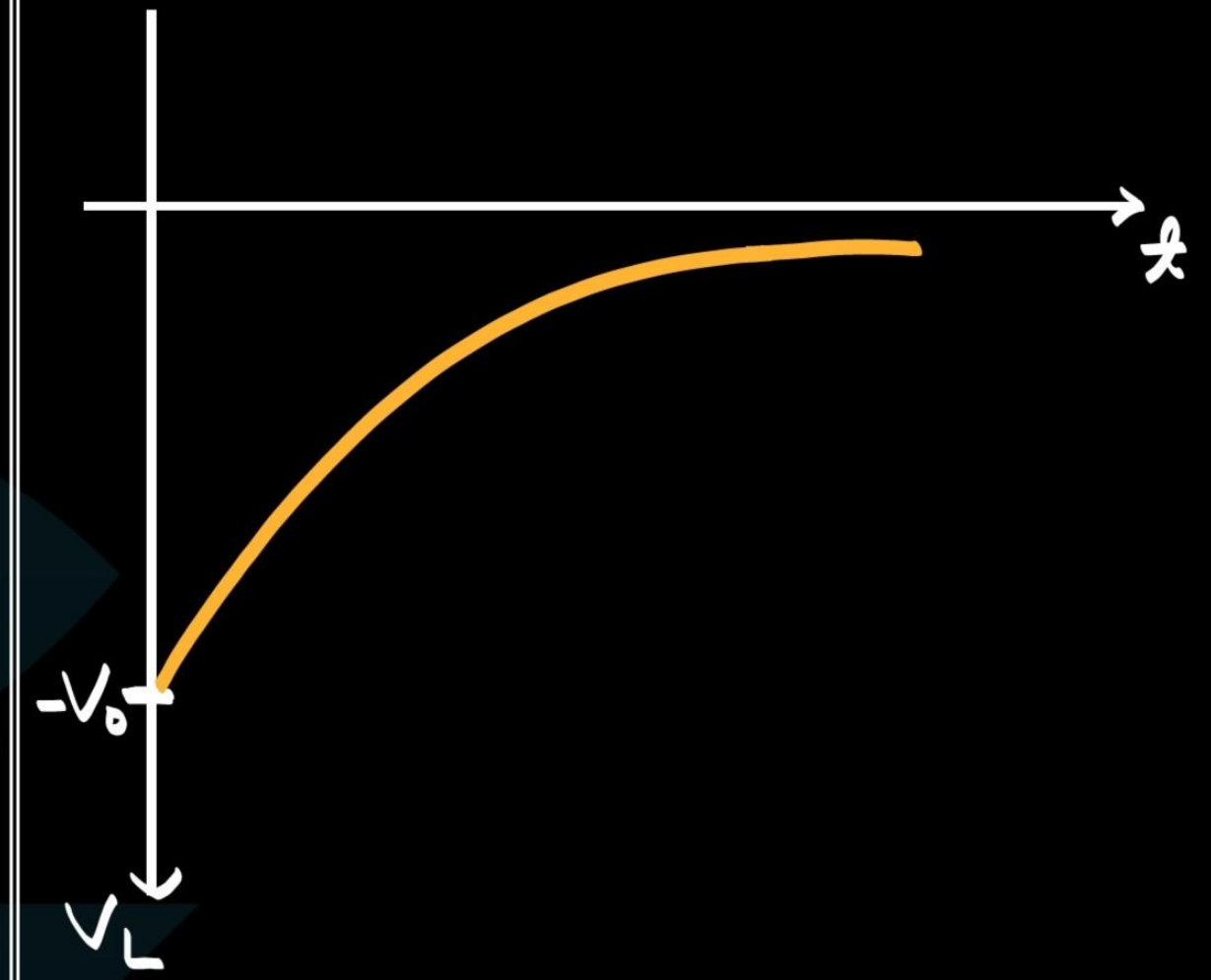

At $t=0$, $V_L = -V_0$


voltage across Resistor

$$V_R = R \cdot i(t)$$

$$= R \cdot I_0 \cdot e^{-Rt/L}$$

$$V_R = V_0 \cdot e^{-Rt/L}$$




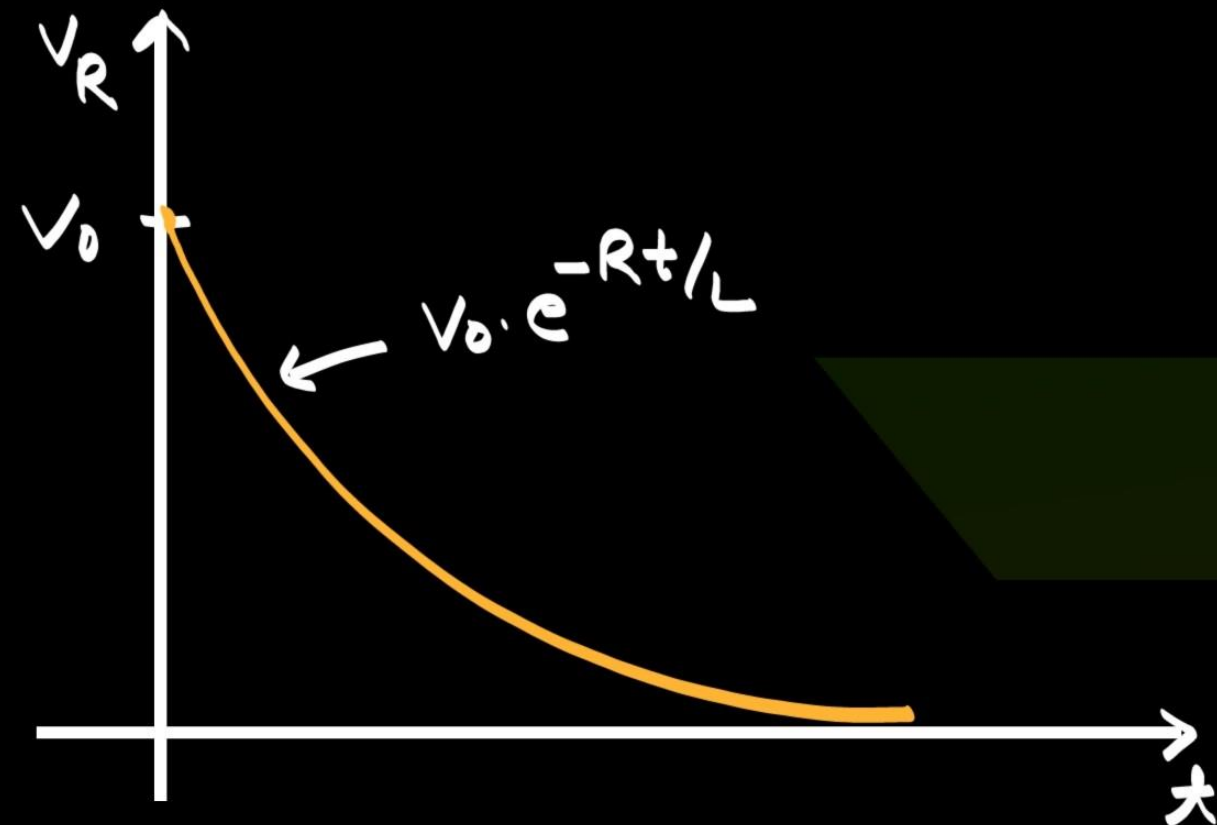

Case-II

RL Circuit with Source

charging

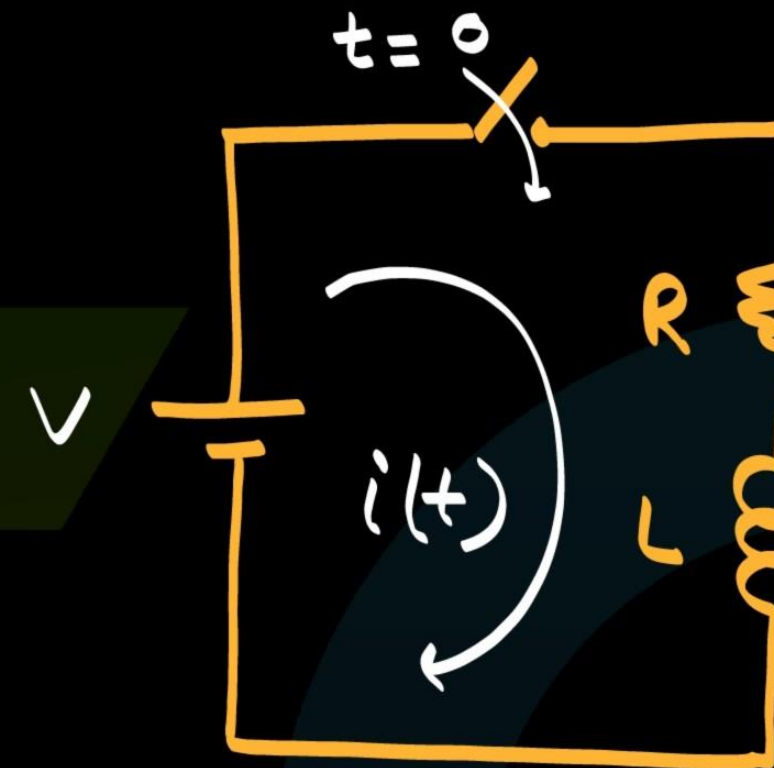

At $t=0 \rightarrow$ switch will connect.

Apply KVL \rightarrow

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

Divide above eqn with $L \rightarrow$

$$\frac{V}{L} = \frac{R}{L} \cdot i + \frac{L}{L} \cdot \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} \cdot i = \frac{V}{L}$$

$$i(t) = C.F. + P.I.$$

transient

steady state



C.F. \rightarrow transient response \rightarrow

$$\frac{di}{dt} + \frac{R}{L} \cdot i = 0$$

After solving this.

$$i(t) = A \cdot e^{-Rt/L} \rightarrow \textcircled{1}$$

$A \rightarrow$ Constant

P.I. \rightarrow steady state

$$i(t) = \frac{V}{R} \rightarrow \textcircled{II}$$

$$i(t) = C.F. + P.I.$$

$$i(t) = A \cdot e^{-Rt/L} + \frac{V}{R}$$

$$At \ t = 0^-, \ i(t) = 0$$

$$t = 0^+, \ i(t) = 0$$

$$t = 0, \ i(t) = 0$$

$$\text{so, } 0 = A \cdot e^0 + \frac{V}{R}$$

$$e^0 = 1$$

$$0 - \frac{V}{R} = A$$

$$i(\infty) = \frac{V}{R}$$

$$A = i(0^+) - i(\infty)$$

so,

$$i(t) = \{i(0^+) - i(\infty)\} e^{-\frac{Rt}{L}} + \frac{V}{R}$$

$$i(t) = (i(0^+) - i(\infty)) e^{-\frac{Rt}{L}} + i(\infty)$$


$$i(t) = \left(0 - \frac{V}{R}\right) e^{-Rt/L} + \frac{V}{R}$$

$$i(t) = \frac{V}{R} (1 - e^{-Rt/L})$$

$$\text{Let } I_0 = \frac{V}{R}$$

$$i(t) = I_0 (1 - e^{-Rt/L})$$



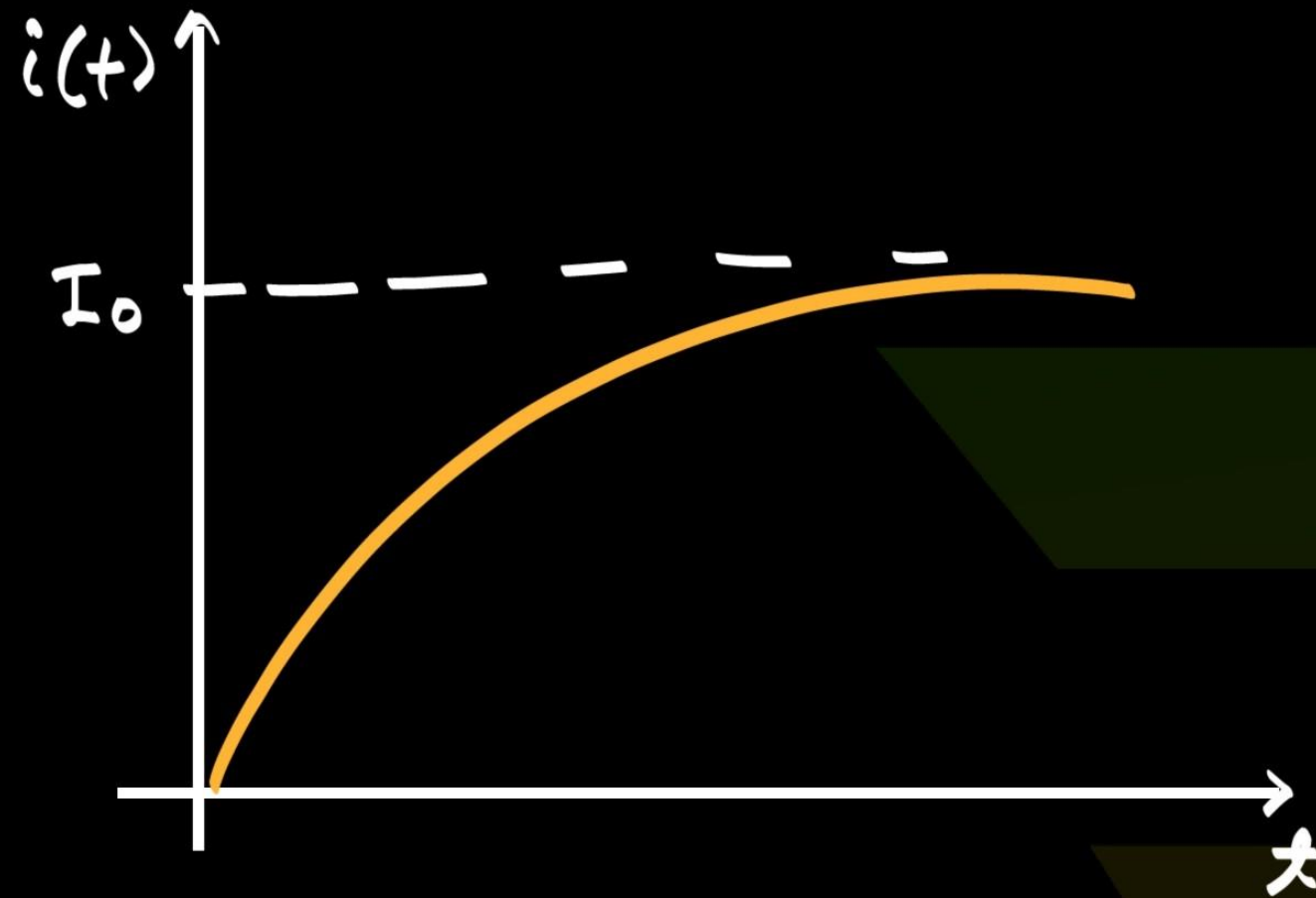

$$i(t) = I_0 (1 - e^{-Rt/L})$$

$$t = \infty$$


$$i(t) = I_0$$

Voltage across Resistor

$$V_R = R \cdot i(t)$$

$$V_R = R \cdot I_0 \cdot (1 - e^{-Rt/L})$$

$$V_R = V_0 \cdot (1 - e^{-Rt/L})$$

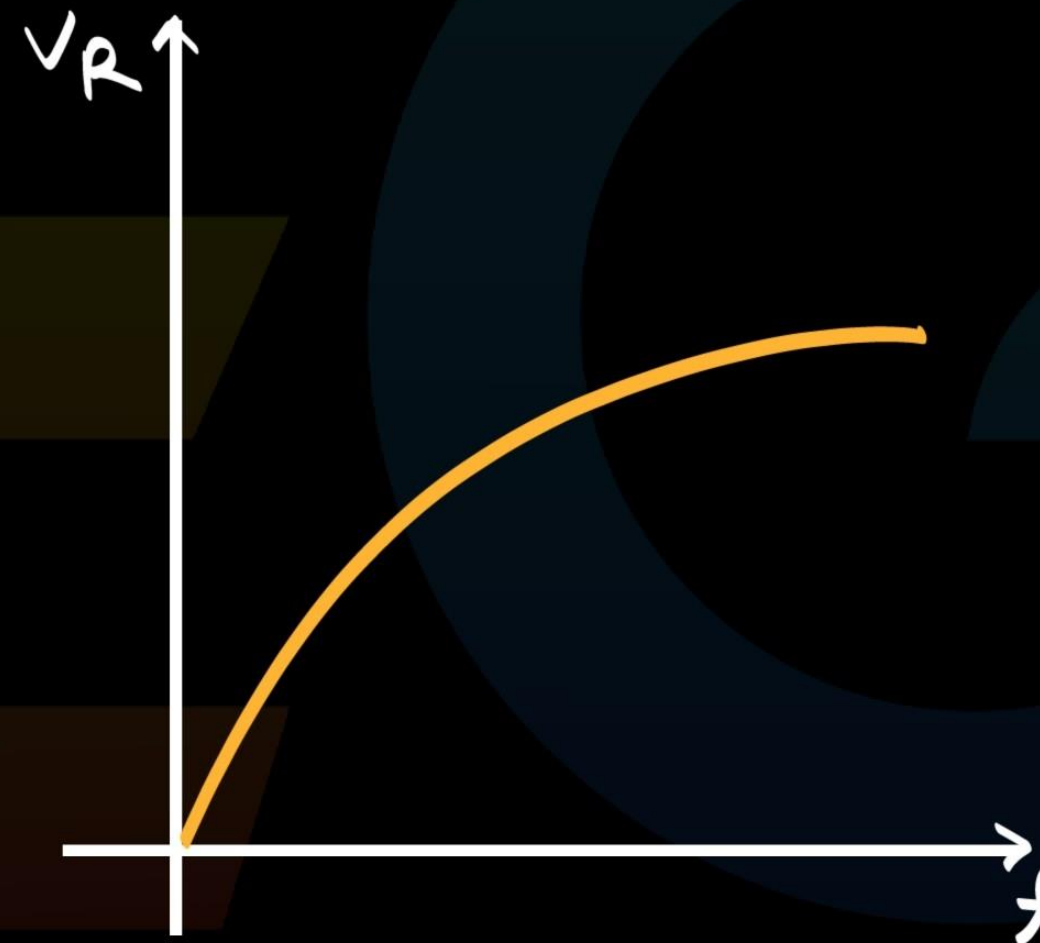

Voltage across inductor.

$$V_L = L \cdot \frac{di(t)}{dt}$$

$$V_L = L \cdot \frac{d}{dt} I_0 (1 - e^{-Rt/L})$$

$$V_L = \cancel{L} \cdot I_0 \left(0 + \frac{R}{\cancel{L}} \cdot e^{-Rt/L} \right)$$

$$V_L = I_0 \cdot R \cdot e^{-Rt/L}$$

$$V_L = V_0 \cdot e^{-Rt/L}$$

$$V_0 = I_0 \cdot R$$

