


## DC transients


Transients present in any circuit due to change in source magnitude or load elements, and it contains energy storing elements.

Energy storing Element  $\rightarrow$  Inductor  $\rightarrow$  mag. form  
 Capacitor  $\rightarrow$  Electrostatic form.

In Pure resistive circuit  $\rightarrow$  Transients are not present.

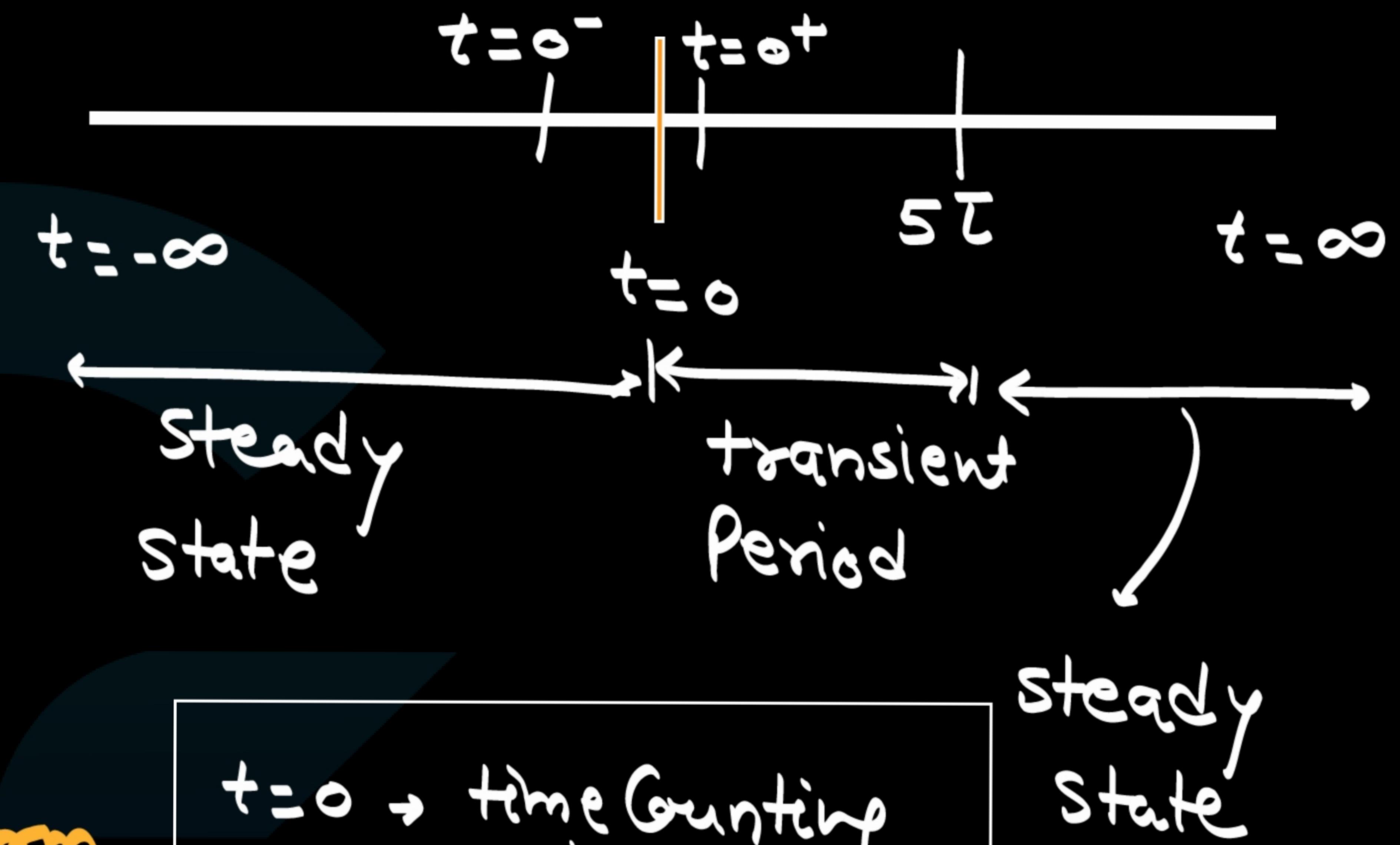Any energy storing element must present in circuit



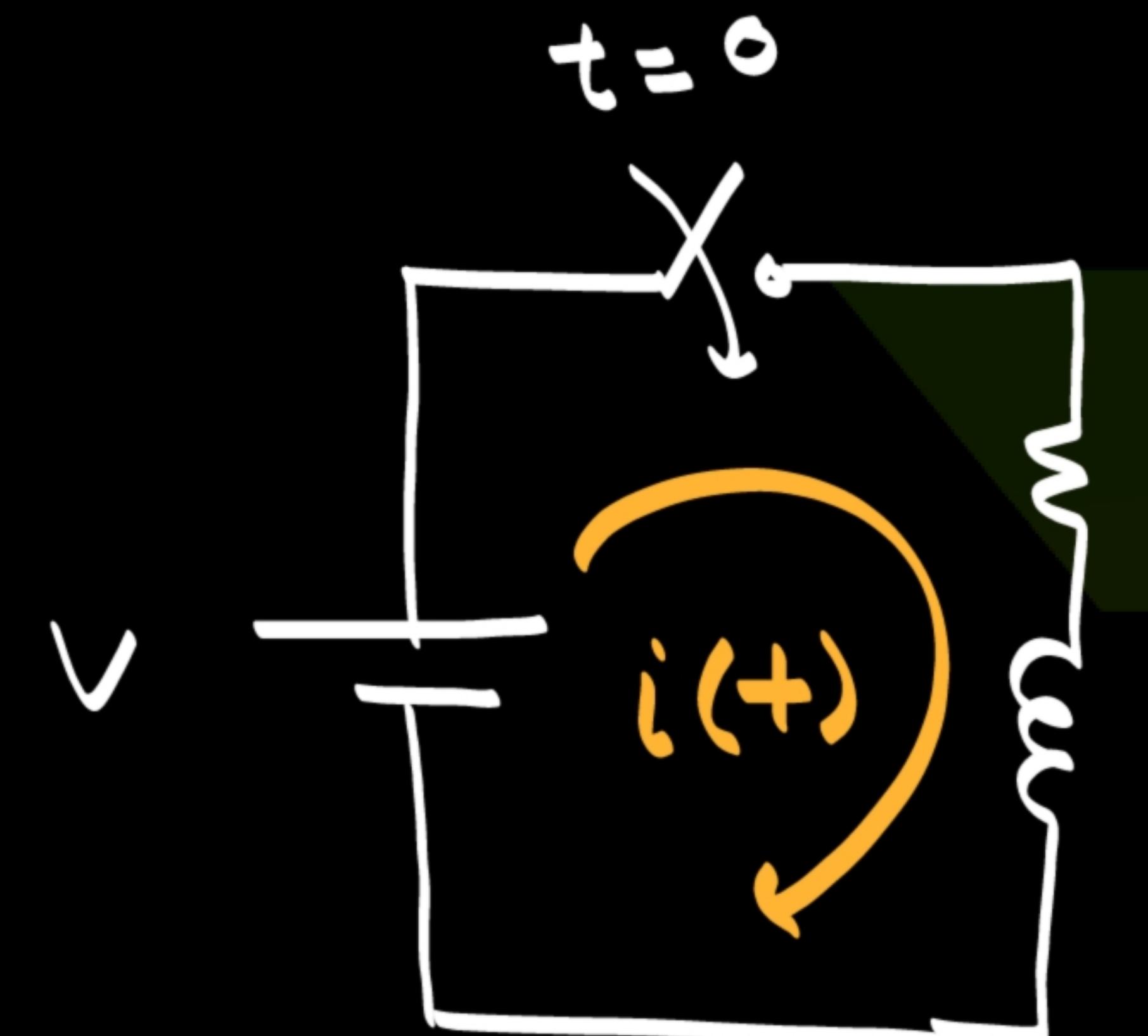**Case Study**
**Case - I**


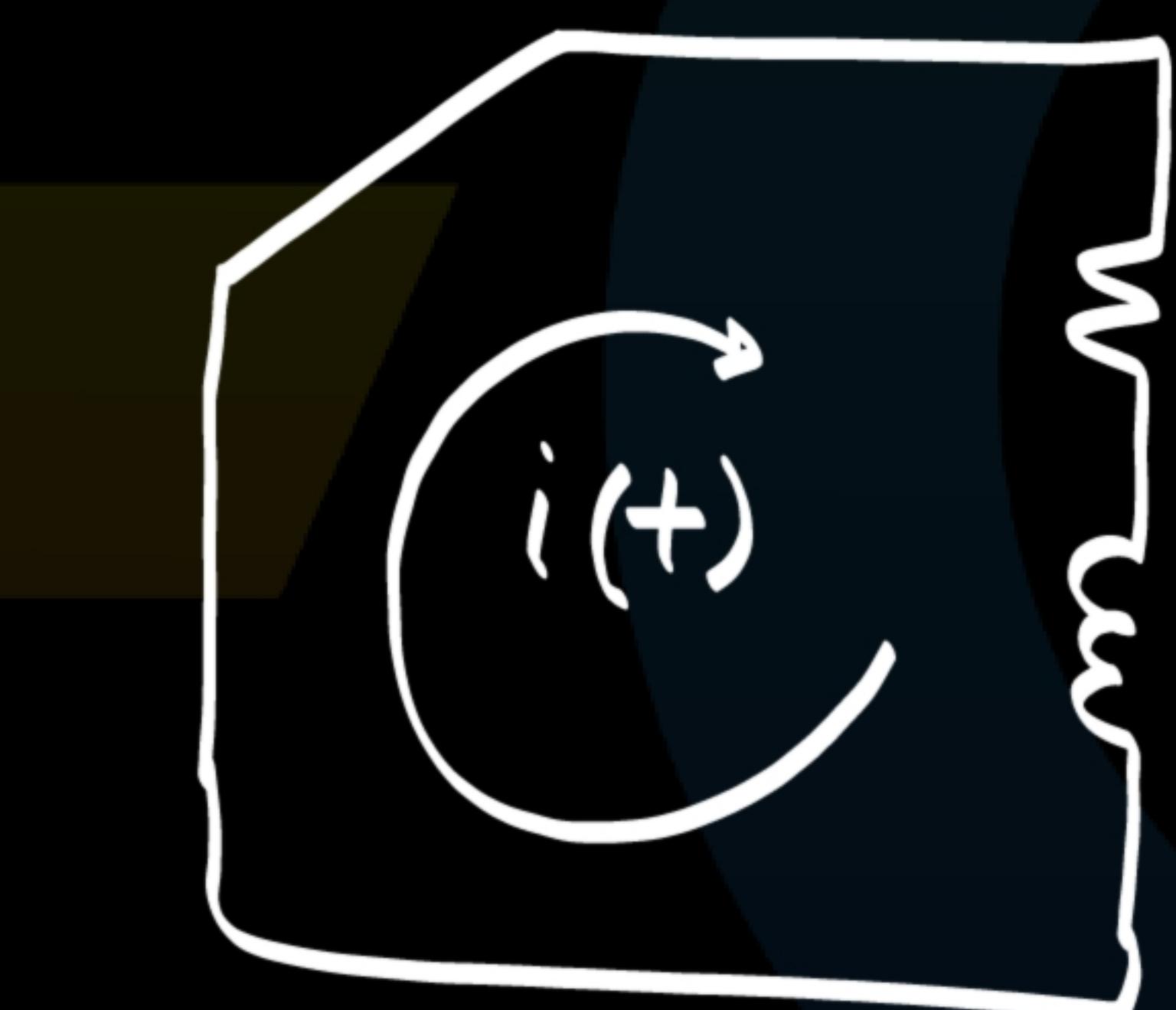
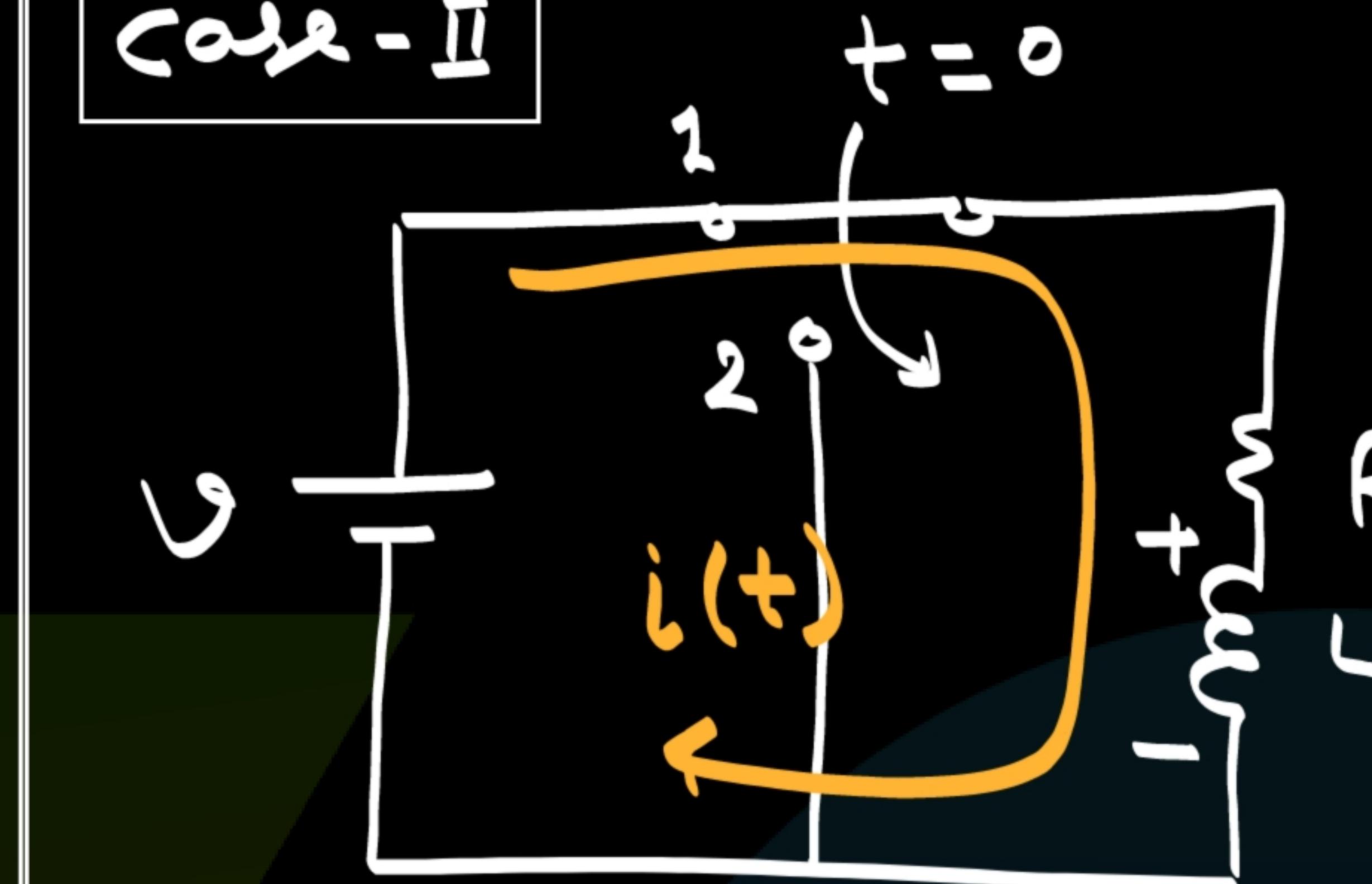
$$t = 0^-, \quad i(+)=0 \text{ Amp}$$

$$t = 0^+, \quad i(+)=0 \text{ Amp}$$

Inductor  $\rightarrow$  open circuit

$$t = \infty, \quad i(+)=\frac{V}{R} \text{ Amperes}$$


Inductor  $\rightarrow$  short circuit.

**Case - II**


$$t = 0^-, \quad i(+)=I_0 \quad \checkmark$$

$$t = 0^+, \quad i(t)=I_0 \quad \checkmark$$

Inductor  $\rightarrow$  Current Source  
 $t = \infty, \quad i(+)=0 \text{ Amp}$  ✓

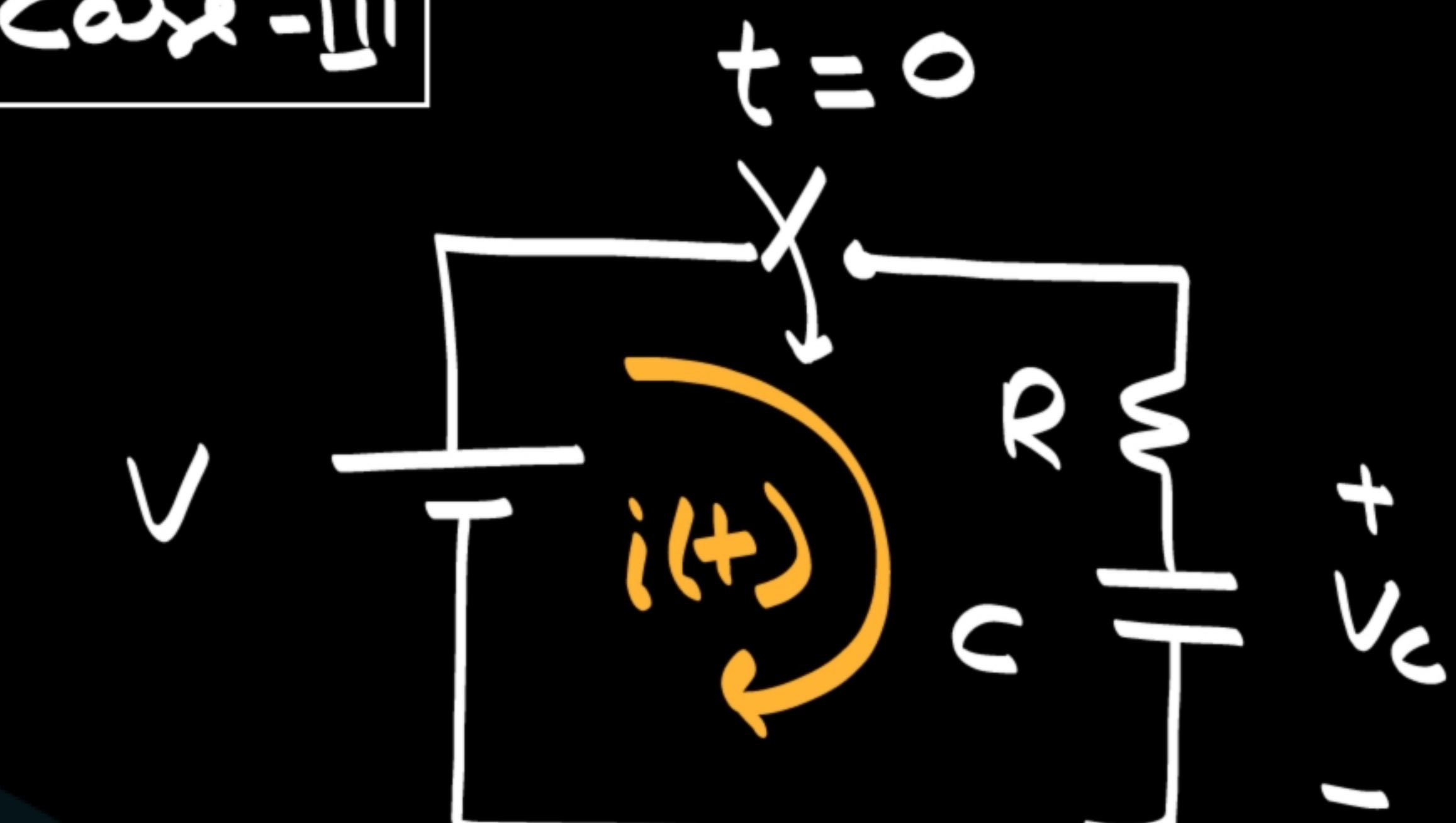**Case - III**


$$\text{At } t = 0^-, \quad V_c(+)=0 \text{ Volt}$$

$$\text{At } t = 0^+, \quad V_c(+)=0 \text{ Volt}$$


Capacitor  $\rightarrow$  Short Circuit.

$$\text{At } t = \infty, \quad V_c(+)=V \text{ volt}$$



$$i(+)=\frac{V-V}{R}$$

$$i(+)=0 \text{ Amp}$$

Capacitor  $\rightarrow$  Open Circuit

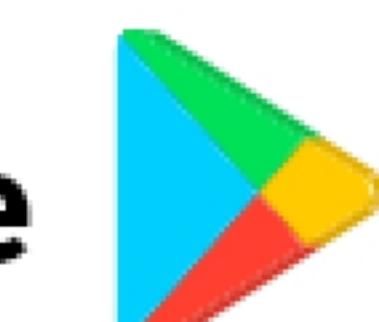

Case-IV

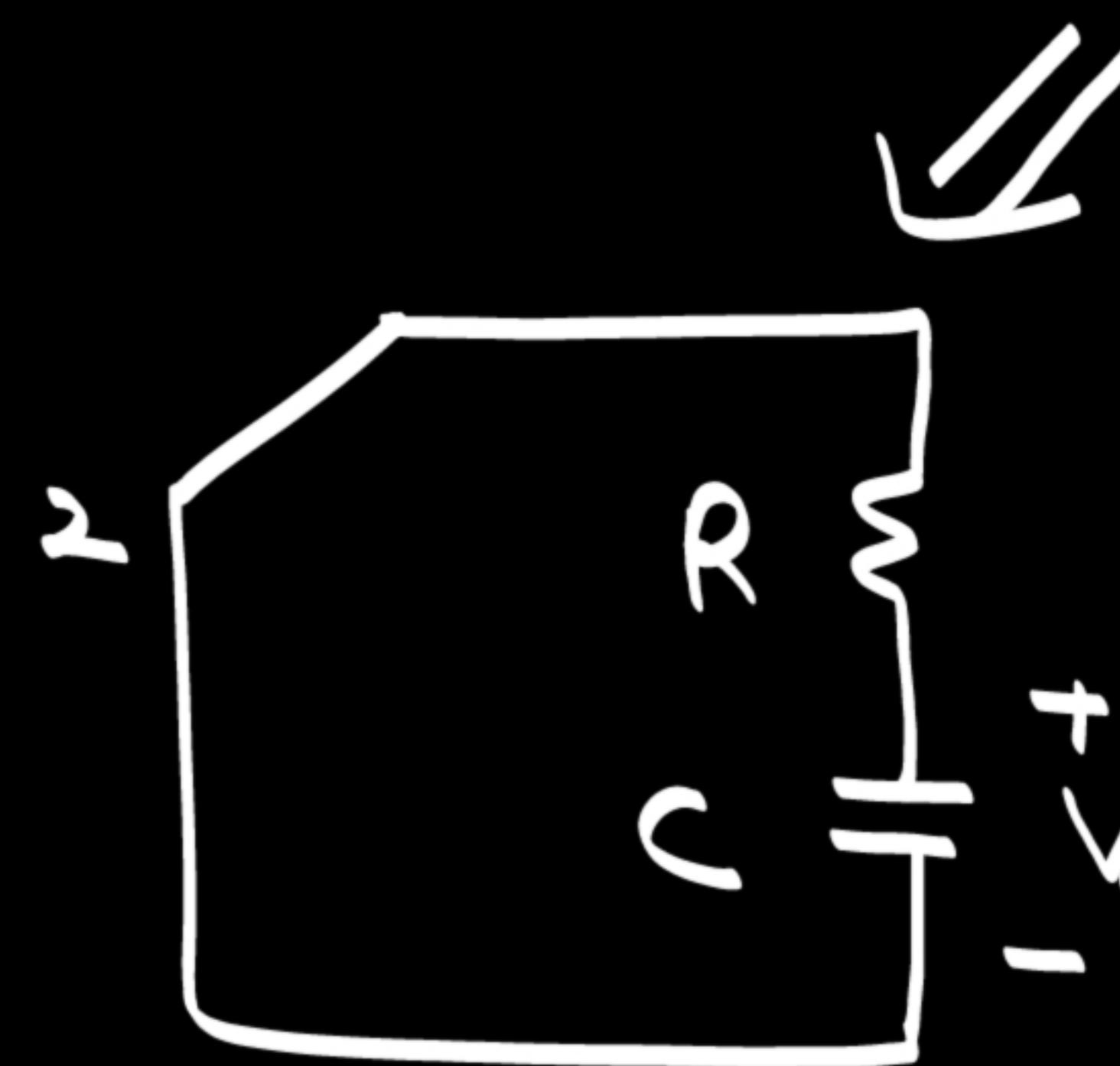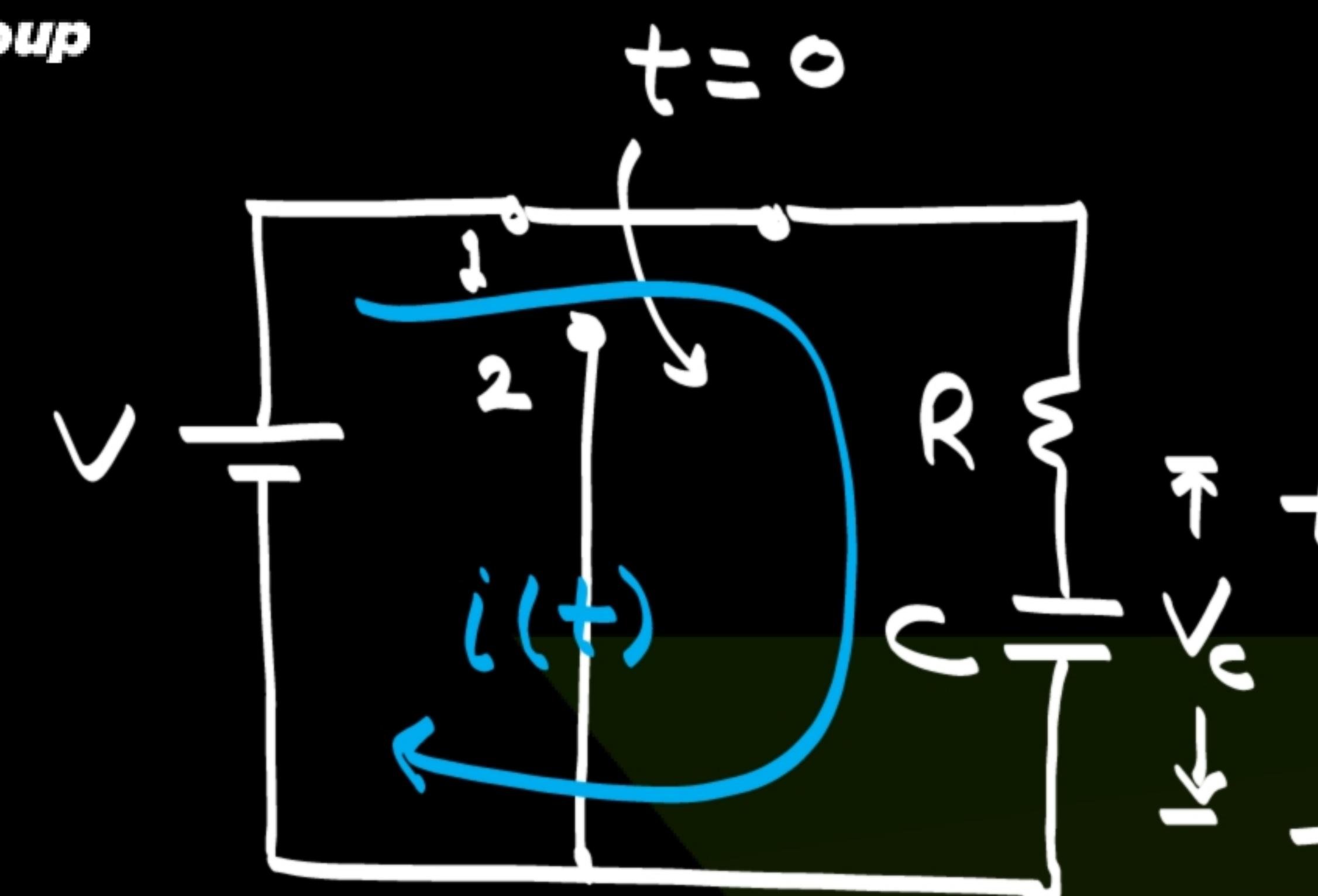

$$\text{At } t = 0^-, \quad V_C(t) = V_0 \\ \text{At } t = 0^+, \quad V_C(t) = V_0$$

Capacitor  $\rightarrow$  Voltage Source

$$t = \infty, \quad V_C(t) = 0$$


Inductor - do not accept change in current.  
Capacitor - do not accept change in voltage.




Case - I

## Source free RL Circuit

Discharging of  
Inductor

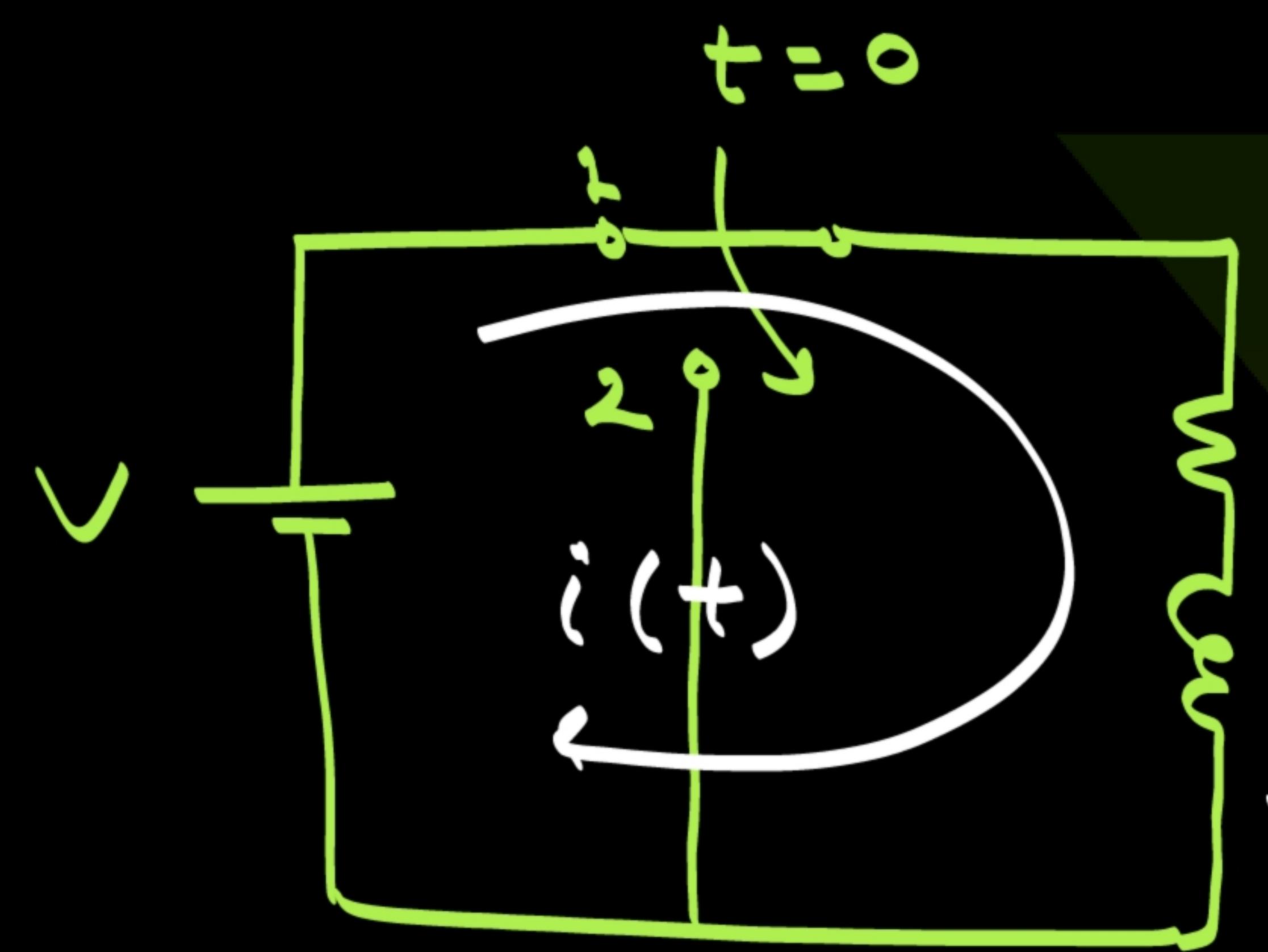
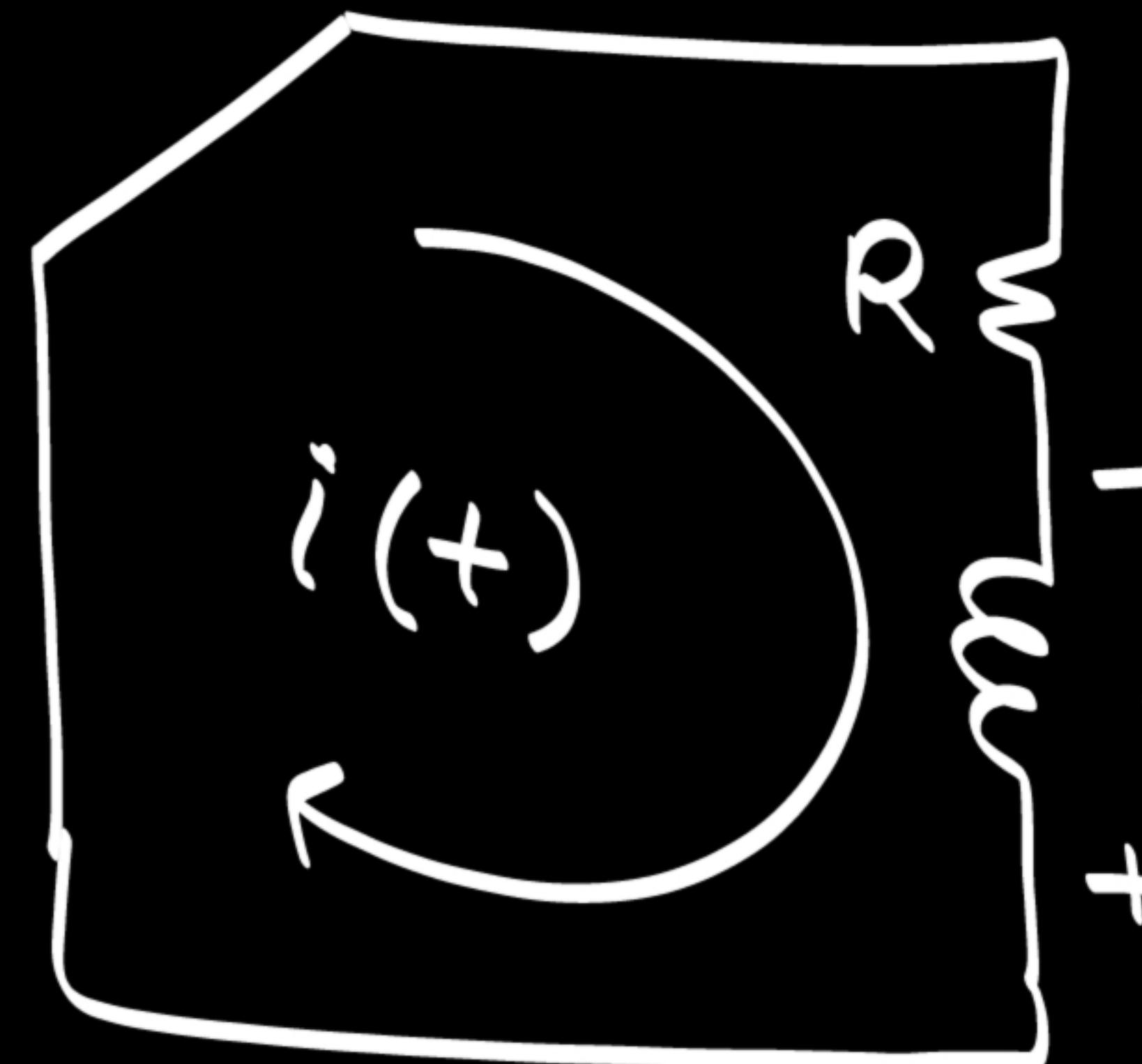
$$\begin{aligned} \text{At } t = 0^- \\ i(t) = I_0 \\ t = 0^+, \\ i(t) = I_0 \\ t = 0 \Rightarrow i(t) = I_0 \end{aligned}$$



At  $t = 0$ , switch is connected to Position 2 →

Apply KVL →

$$R \cdot i(t) + L \cdot \frac{di(t)}{dt} = 0$$

$$R \cdot i(t) = -L \cdot \frac{di(t)}{dt}$$

$$-\frac{R}{L} \cdot dt = \frac{di(t)}{i(t)}$$

$$\int_0^t -\frac{R}{L} \cdot dt = \int_{I_0}^{i(t)} \frac{di(t)}{i(t)}$$

$$-\frac{R}{L} \cdot t = \left[ \log i(t) \right]_{I_0}^{i(t)}$$

$$-\frac{R}{L} \cdot t = \log(i(t))$$

$$-\log(I_0)$$


$$-\frac{R}{L} \cdot t = \log\left(\frac{i(t)}{I_0}\right)$$

take Antilog

$$\frac{i(t)}{I_0} = e^{-Rt/L}$$

$$i(t) = I_0 \cdot e^{-Rt/L}$$



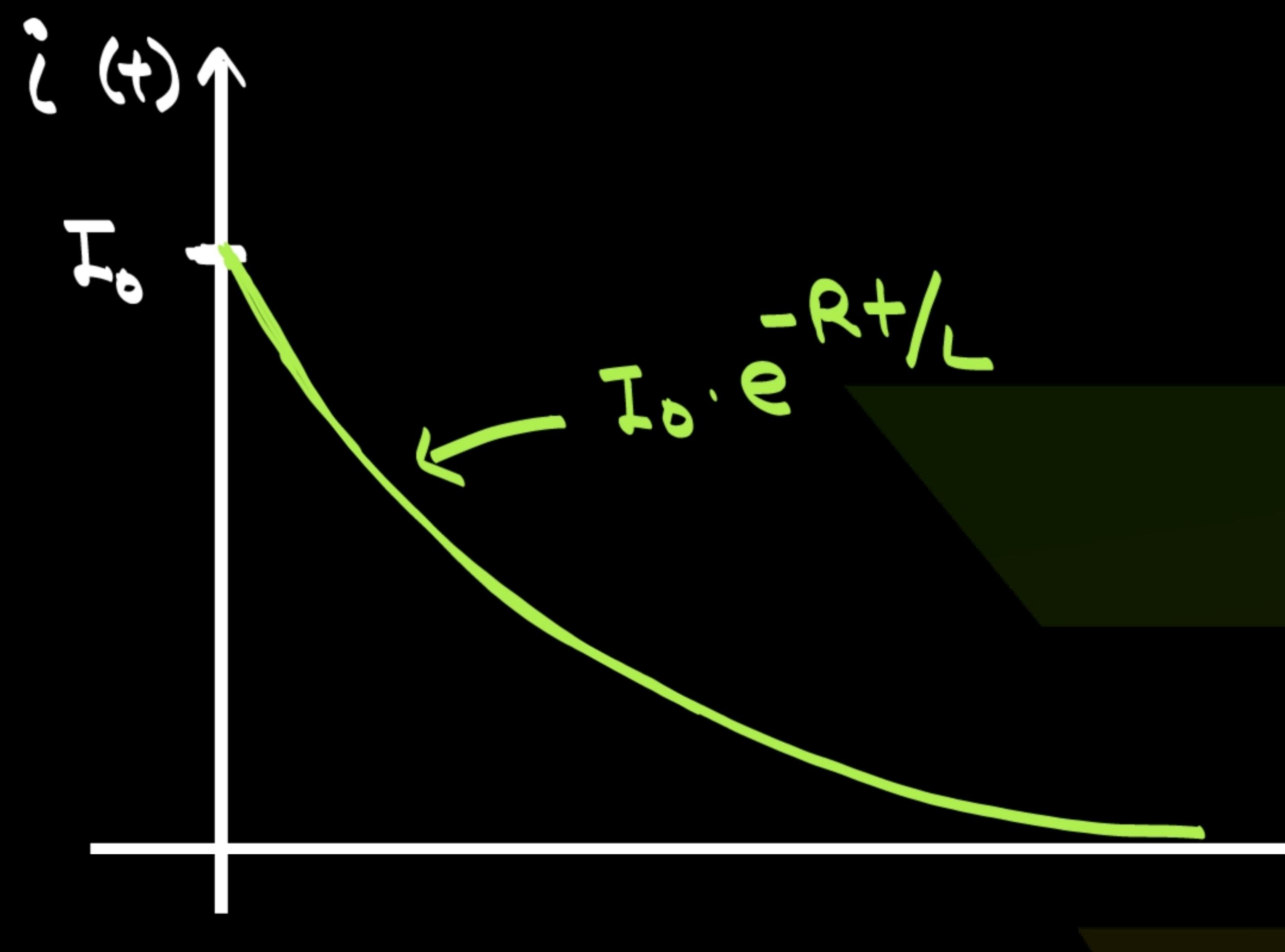

$$i(t) = I_0 \cdot e^{-Rt/L}$$

$$\text{At } t=0, \rightarrow i(t) = I_0$$

$$\text{At } t=\infty, \rightarrow i(t) = 0$$

Voltage across inductor -

$$V_L = L \cdot \frac{di(t)}{dt}$$


$$V_L = L \cdot \frac{d}{dt} I_0 \cdot e^{-Rt/L}$$

$$= I_0 \cdot L \cdot \left( -\frac{R}{L} \right) \cdot e^{-Rt/L}$$

$$V_L = -I_0 R e^{-Rt/L}$$

$$\text{let } (V_0 = I_0 R)$$

$$V_L = -V_0 \cdot e^{-Rt/L}$$


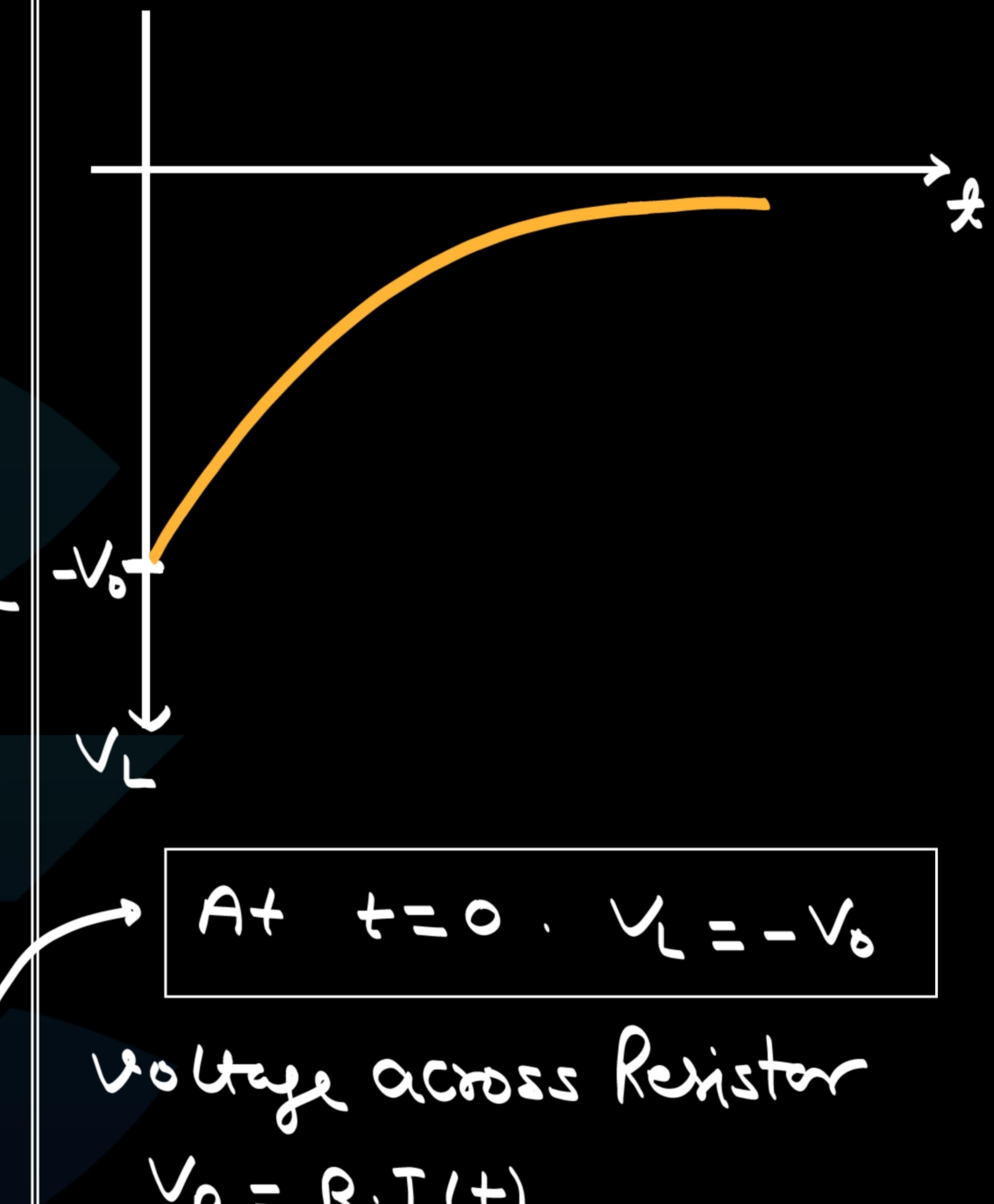


$$V_R = R \cdot I(t)$$

$$= R \cdot I_0 \cdot e^{-Rt/L}$$

$$V_R = V_0 \cdot e^{-Rt/L}$$

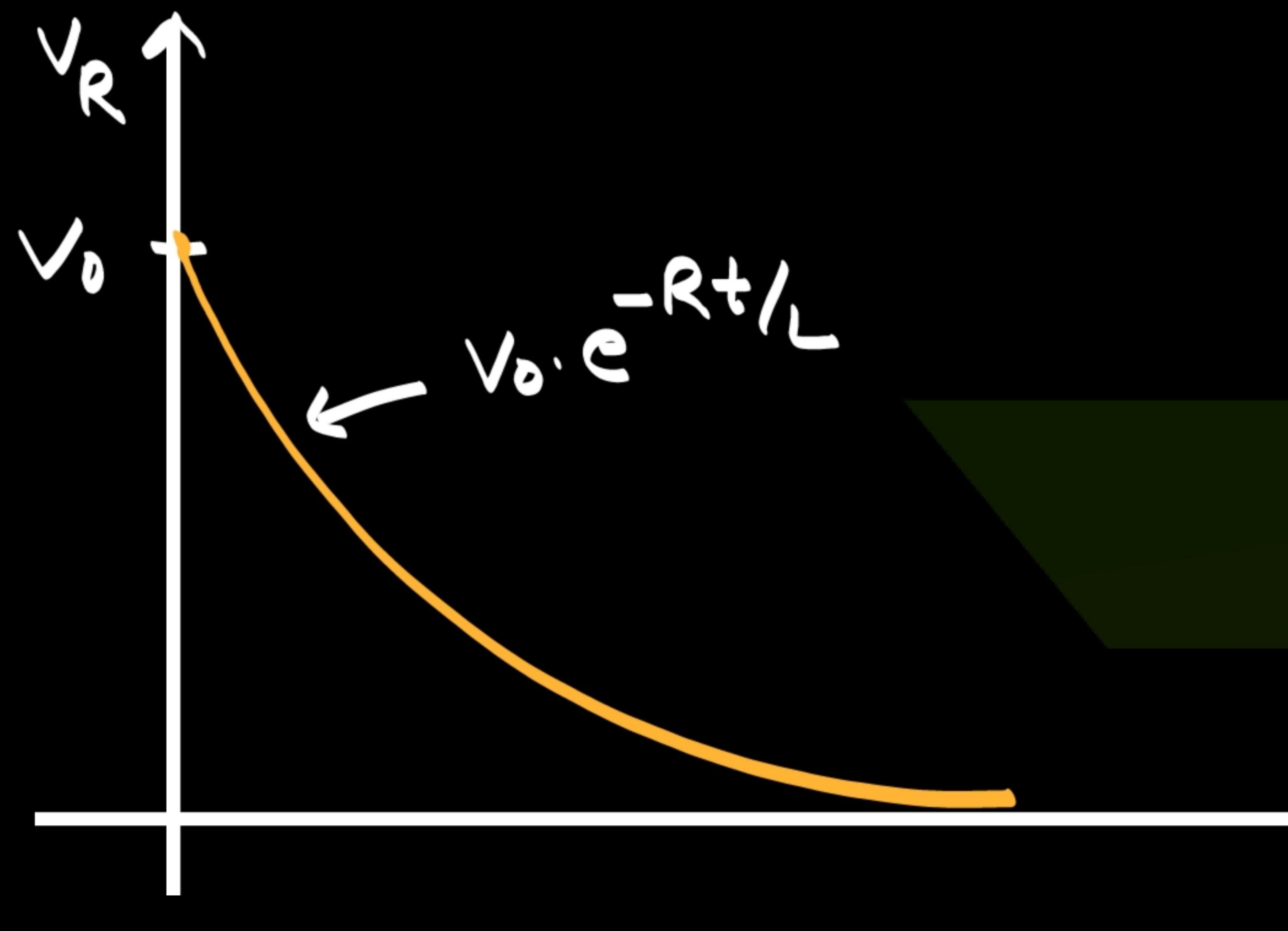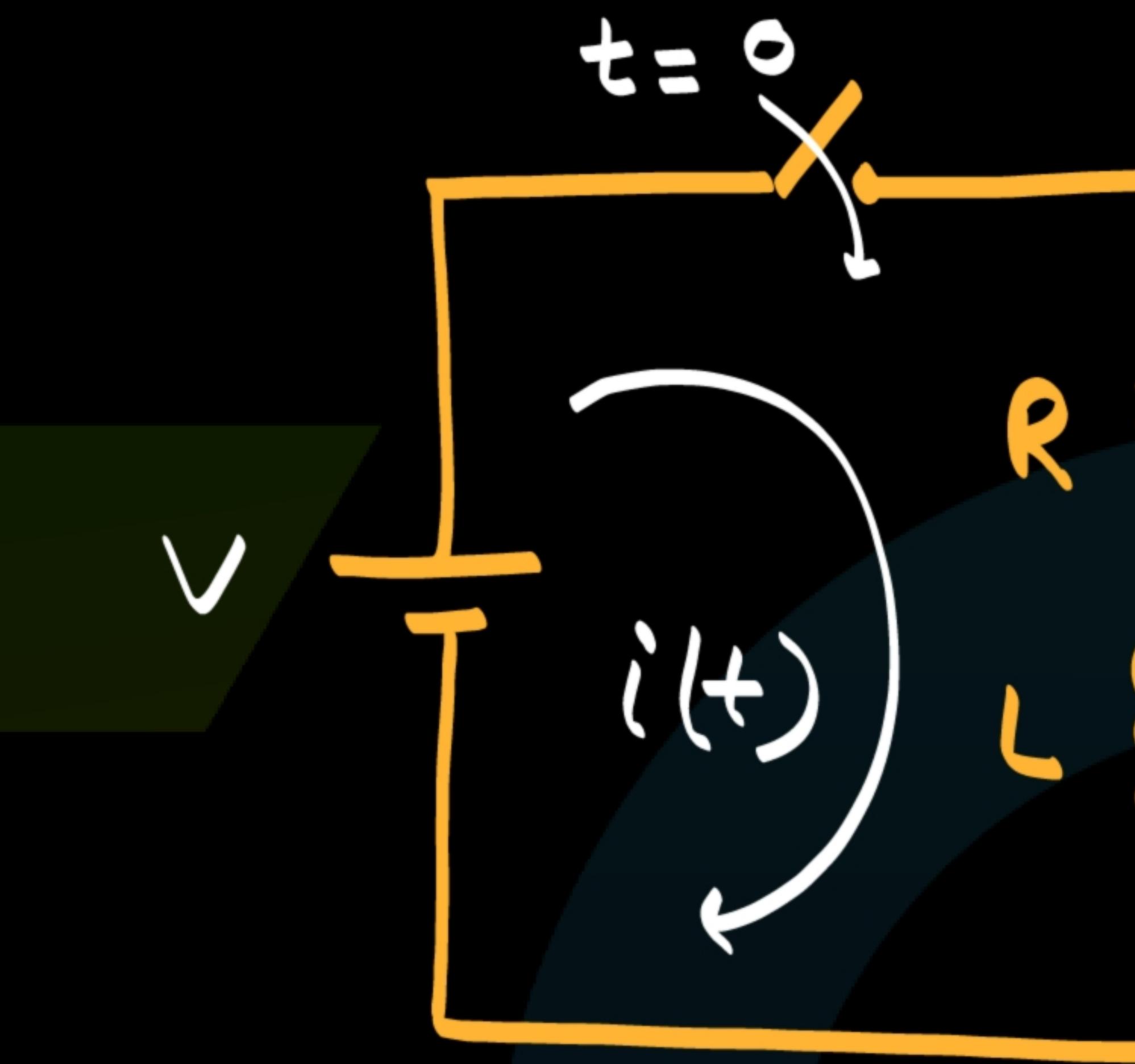


**Case-II**
**RL Circuit with Source**
**Charging**


At  $t=0 \rightarrow$  switch will connect.

Apply KVL  $\rightarrow$

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

$$V = R \cdot i + L \cdot \frac{di}{dt}$$

Divide above eqn with  $L \rightarrow$

$$\frac{V}{L} = \frac{R}{L} \cdot i + \frac{1}{L} \cdot \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L} \cdot i = \frac{V}{L}$$

$$i(t) = C.F. + P.I.$$

transient

steady state



C.F.  $\rightarrow$  transient response  $\rightarrow$

$$\frac{di}{dt} + \frac{R}{L} \cdot i = 0$$

After solving this.

$$i(t) = A \cdot e^{-Rt/L} \rightarrow \textcircled{I}$$

$A \rightarrow$  Constant

P.I.  $\rightarrow$  steady state

$$i(t) = \frac{V}{R} \rightarrow \textcircled{II}$$

$$i(t) = C.F. + P.I.$$

$$i(t) = A \cdot e^{-Rt/L} + \frac{V}{R}$$

$$\text{At } t = 0^-, i(t) = 0$$

$$t = 0^+, i(t) = 0$$

$$t = \infty, i(t) = 0$$

$$\text{So, } 0 = A \cdot e^0 + \frac{V}{R}$$

$$e^0 = 1$$

$$0 - \frac{V}{R} = A$$

$$i(\infty) = \frac{V}{R}$$

$$A = i(0^+) - i(\infty)$$

so,

$$i(t) = \left\{ i(0^+) - i(\infty) \right\} e^{-\frac{Rt}{L}} + \frac{V}{R}$$

$$i(t) = \left( i(0^+) - i(\infty) \right) e^{-\frac{Rt}{L}} + i(\infty)$$


$$i(t) = \left( 0 - \frac{V}{R} \right) e^{-\frac{Rt}{L}} + \frac{V}{R}$$

$$i(t) = \frac{V}{R} \left( 1 - e^{-\frac{Rt}{L}} \right)$$

$$\text{Let } I_0 = \frac{V}{R}$$
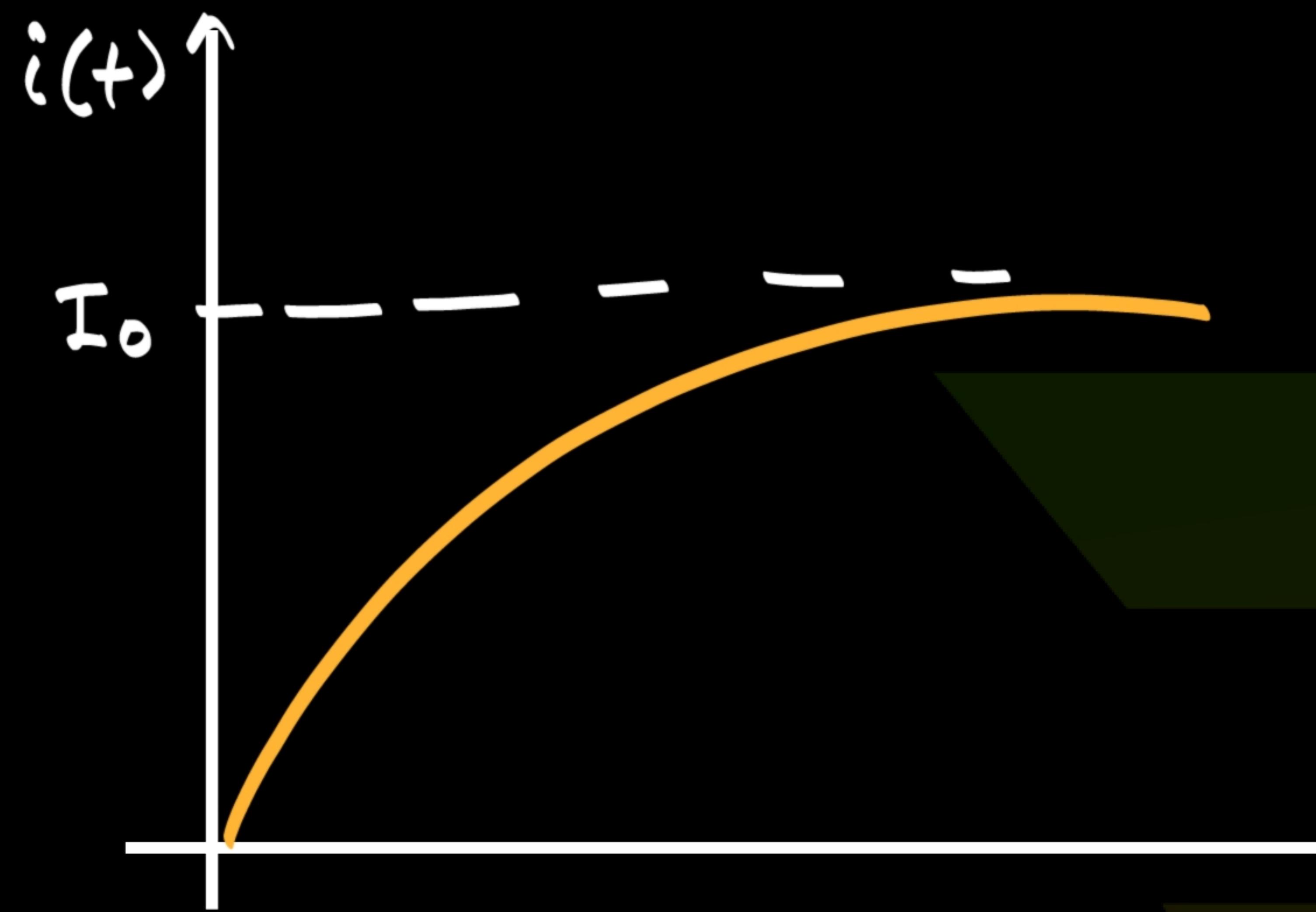
$$i(t) = I_0 \left( 1 - e^{-\frac{Rt}{L}} \right)$$





$$i(t) = I_0(1 - e^{-Rt/L})$$

 $\tau = \infty$ 


$$i(t) = I_0$$

### Voltage across Resistor.

$$V_R = R \cdot i(t)$$

$$V_R = R \cdot I_0 \cdot (1 - e^{-Rt/L})$$

$$V_R = V_0 \cdot (1 - e^{-Rt/L})$$

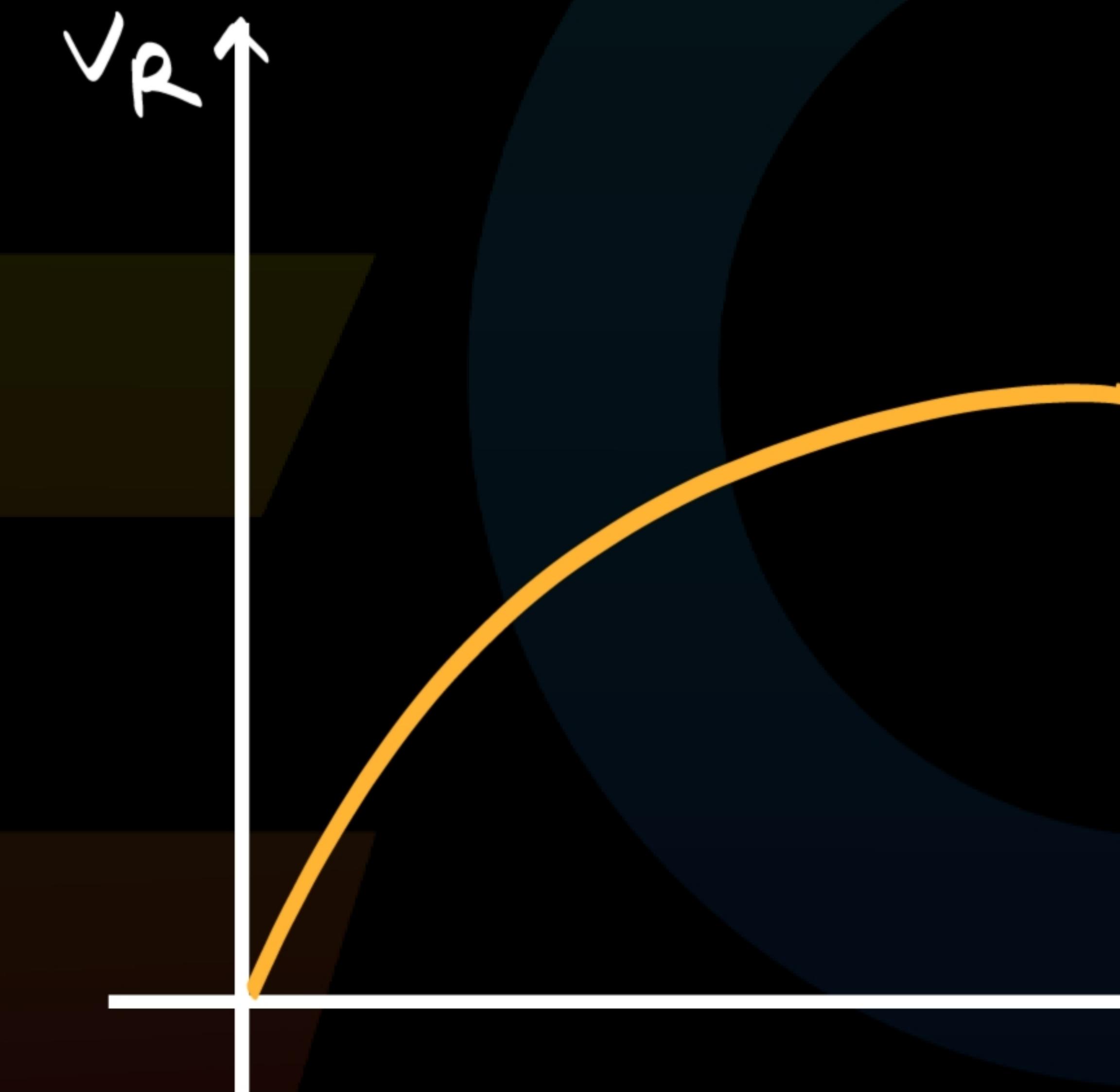 $V_R$ 
 $t$ 


### Voltage across inductor.

$$V_L = L \cdot \frac{di(t)}{dt}$$

$$V_L = L \cdot \frac{d}{dt} I_0 (1 - e^{-Rt/L})$$

$$V_L = L \cdot I_0 \left( 0 + \frac{R}{L} \cdot e^{-Rt/L} \right)$$

$$V_L = I_0 \cdot R \cdot e^{-Rt/L}$$

$$V_L = V_0 \cdot e^{-Rt/L}$$

$$V_0 = I_0 \cdot R$$

